

ECE 281
Electrical Circuits and Instrumentation + Laboratory
Fall 2016/2017
LAB # 5-Supplement

31.10.2016

Objective:

1. Learn the use of a rheostat

1. Learn the use of a rheostat (15 Points)

Rheostat: Any device that regulates (controls) current flow is called as a rheostat. A potentiometer can be used as a rheostat if it is connected properly in a circuit.

Procedure:

1. Adjust potentiometer to middle when you measure resistance between 1-3
2. Construct the circuit shown in Figure 1 (In this circuit, we take $R_1 = 1k\Omega$ and $V_S = 10V$ DC. We also use a potentiometer whose nominal value is $10k\Omega$). Connect only one of the constant terminal (terminal 1) and the variable terminal (terminal 3) of the potentiometer to the circuit while leaving the other constant terminal (terminal 2) open (don't connect this terminal to anywhere).

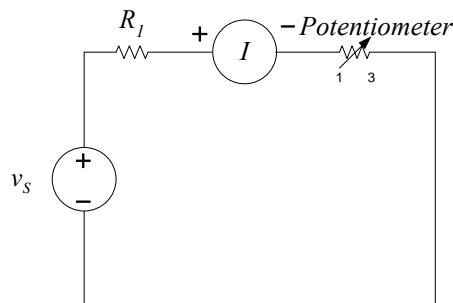


Figure 1: Circuit diagram for current measurement over rheostat

3. Measure current, according to your reading over the Ampermeter.
4. Measure current two more times clockwise and counter-clockwise

Turning direction	Clockwise	Counter-clockwise	Mid-point
Current value (I)			

Table 1: Current measurements

Questions:

- How does the current varies when the shaft is moved clockwise?
- How does the current varies when the shaft is moved counter-clockwise?
- What is the use of rheostat?