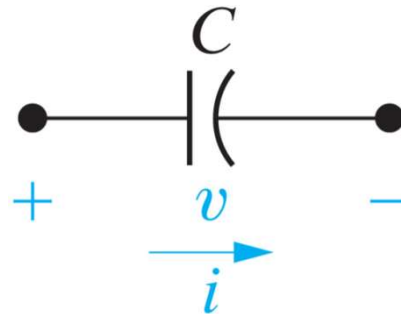


# Capacitor



- Parallel plates, separated by an insulator, so no charge flows between the plates. Impose a time-varying voltage drop:
  - time-varying electric field
  - time-varying displacement current




- Capacitor equation: 
$$i(t) = C \frac{dv(t)}{dt}$$

- Units:  $v(t)$  is volts,  $i(t)$  is amps, and  $C$  is farads [F]




Look at the capacitor equation again:

$$i(t) = C \frac{dv(t)}{dt}$$

Suppose  $v(t)$  is constant. Then  $i(t) =$

-  A. 0
-  B.  $\infty$
-  C. a constant

So, if the voltage drop across the capacitor is constant, its current is 0, so the capacitor can be replaced by

-  A. a short circuit
-  B. an open circuit
-  C. a constant

# Capacitor




- **If the voltage drop across a capacitor is constant, the current is 0, so the capacitor can be replaced by an OPEN CIRCUIT.**
- Look at the capacitor equation again:  $i(t) = C \frac{dv(t)}{dt}$
- Suppose there is a discontinuity in  $v(t)$  – that is, at some value of  $t$ , the voltage jumps instantaneously. At this value of  $t$ , the derivative of the voltage is infinite. Therefore the current is infinite! NOT POSSIBLE.
- **Thus, the voltage drop across a capacitor is continuous for all time.**

The voltage drop across a capacitor is described as

$$v(t) = V_o, \quad t < 0$$

$$v(t) = 15e^{-250t} - 10e^{-1000t} \text{ V}, \quad t \geq 0$$

This expression for the capacitor voltage is valid only if the value of  $V_o$  is

-  A. 0 V
-  B. 25 V
-  C. 5 V

# Capacitor

- The equation for voltage in terms of current:

$$i(t) = C \frac{dv(t)}{dt} \quad \Rightarrow \quad i(t)dt = Cdv(t)$$

$$\Rightarrow \int_{t_o}^t i(\tau)d\tau = C \int_{v(t_o)}^{v(t)} dx$$

$$\Rightarrow v(t) = \frac{1}{C} \int_{t_o}^t i(\tau)d\tau + v(t_o)$$

# Capacitor

- Power and energy

$$p(t) = v(t)i(t) = Cv(t)\frac{dv(t)}{dt} \quad (\text{passive sign convention!})$$

$$p(t) = \frac{dw(t)}{dt} = Cv(t)\frac{dv(t)}{dt}$$

$$\Rightarrow dw(\tau) = Cv(\tau)dv(\tau)$$

$$\Rightarrow \int_0^{w(t)} dx = C \int_0^{v(t)} y(\tau)d\tau$$

$$\Rightarrow w(t) = \frac{1}{2} Cv(t)^2$$

# Capacitor

- Capacitors, like inductors, are **energy storage devices!**
  - If the initial voltage drop across the capacitor is non-zero, the capacitor is storing energy.




Suppose the initial voltage drop across a  $4 \mu\text{F}$  capacitor is  $10 \text{ V}$ . The initial energy stored in the capacitor is

- X** A.  $400 \mu\text{J}$
- ✓** B.  $200 \mu\text{J}$
- X** C.  $20 \mu\text{J}$

# Capacitor

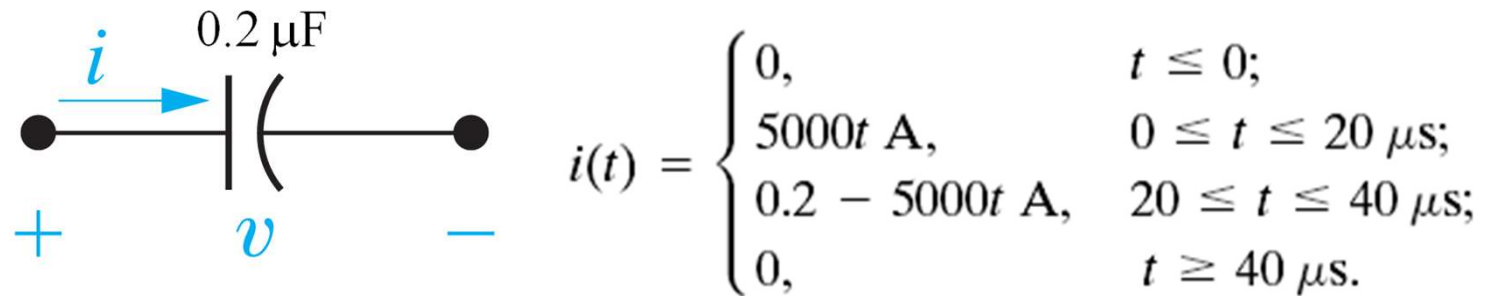- Example 6.5 – find the voltage, power, and energy



For  $t < 0$ :

$$v(t) = 0 \text{ V}; \quad p(t) = 0 \text{ W}; \quad w(t) = 0 \text{ J}$$

For  $0 \leq t \leq 20 \mu\text{s}$ :

$$v(t) = \frac{1}{0.2\mu} \int_0^t 5000x \, dx + v(0) = \frac{1}{0.2\mu} \frac{5000x^2}{2} \Big|_0^t = 12.5 \times 10^9 t^2 \text{ V}$$


$$p(t) = v(t)i(t) = (12.5 \times 10^9 t^2)(5000t) = 62.5 \times 10^{12} t^3 \text{ W}$$

$$w(t) = \frac{1}{2}(0.2\mu)(12.5 \times 10^9 t^2)^2 = 15.625 \times 10^{12} t^4 \text{ J}$$

$$\text{At } t = 20\mu\text{s}, \quad v(20\mu\text{s}) = 12.5 \times 10^9 (20\mu)^2 = 5 \text{ V}$$

# Capacitor

- Example 6.5, continued

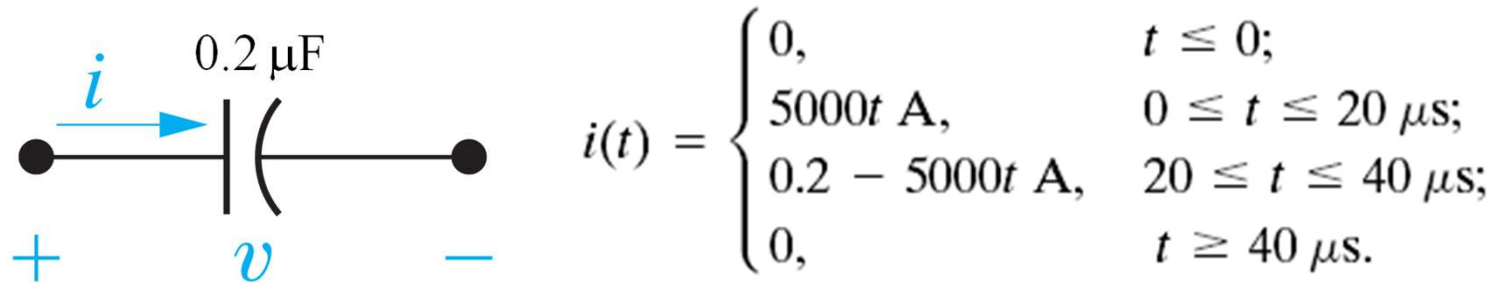

For  $20 \mu\text{s} \leq t \leq 40 \mu\text{s}$  :

$$v(t) = \frac{1}{0.2 \mu} \int_{20 \mu}^t (0.2 - 5000x) dx + v(20 \mu)$$

$$= \frac{1}{0.2 \mu} \left[ 0.2x - \frac{5000x^2}{2} \right]_0^t + 5$$


$$= (10^6 t - 12.5 \times 10^9 t^2 - 10) \text{ V}$$

$$p(t) = v(t)i(t); \quad w(t) = \frac{1}{2} C v(t)^2$$

$$\text{At } t = 40 \mu\text{s}, \quad v(40 \mu\text{s}) = [10^6(40 \mu) - 12.5 \times 10^9(40 \mu)^2 - 10] = 10 \text{ V}$$

# Capacitor

- Example 6.5, continued

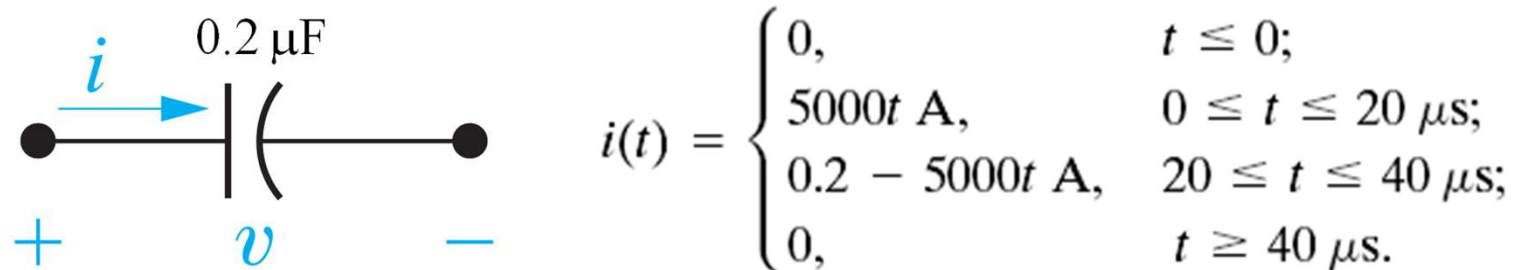

For  $t \geq 40\mu\text{s}$ :

$$v(t) = \frac{1}{0.2\mu} \int_{40\mu}^t 0 \, dx + v(40\mu) = 10 \text{ V}$$





$$p(t) = v(t)i(t) = 0 \text{ W}$$

$$w(t) = \frac{1}{2}(0.2\mu)(10)^2 = 10\mu\text{J!}$$


During the interval between 0 and  $40\mu\text{s}$ , the power is positive (absorbed), energy is stored and “trapped” by the capacitor, so even when the current goes to 0, the voltage stays at 10 V and the energy is non-zero.

# Capacitor

- Example 6.5, continued

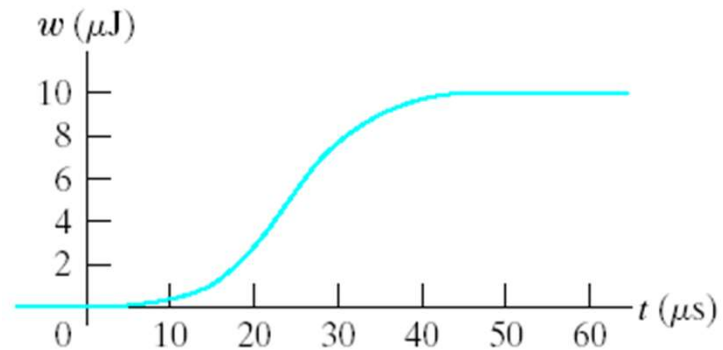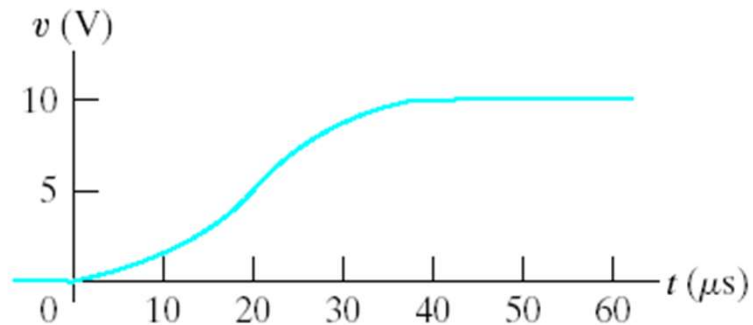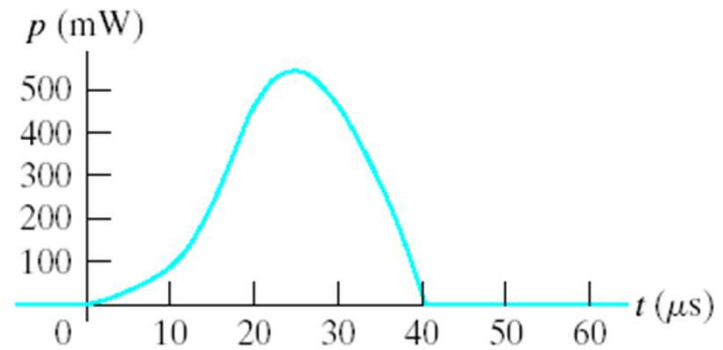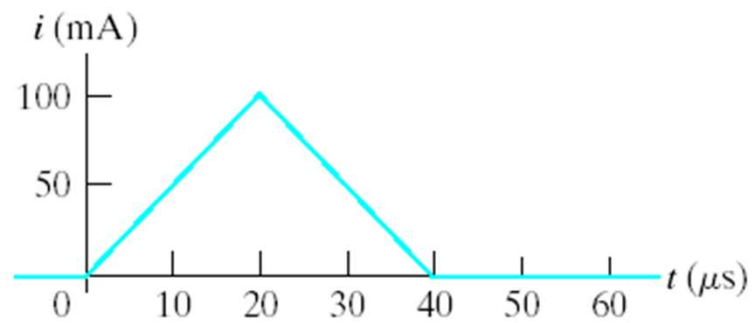


# Capacitors in series and parallel

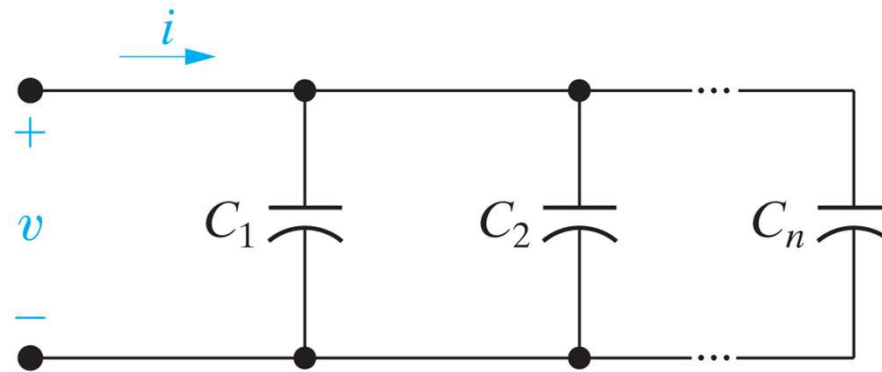

$$\begin{aligned} \text{KCL:} \quad i &= i_1 + i_2 + i_3 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt} \\ &= (C_1 + C_2 + C_3) \frac{dv}{dt} = C_{eq} \frac{dv}{dt} \end{aligned}$$

Capacitors in parallel ADD.


# Capacitors in series and parallel

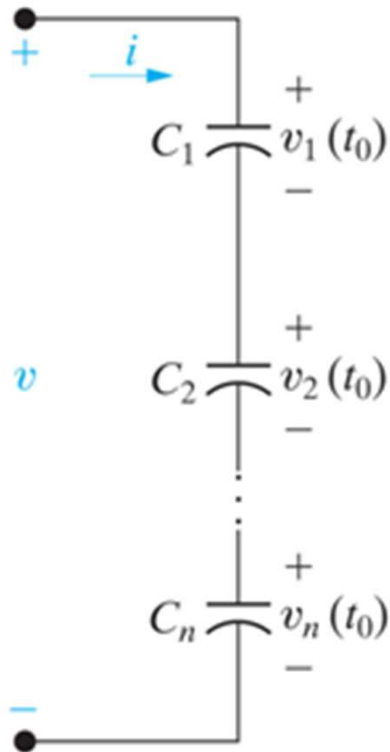

$$\begin{aligned} \text{KVL: } v &= v_1 + v_2 + v_3 = \frac{1}{C_1} \int_{t_0}^t i(\tau) d\tau + v_1(t_0) \\ &+ \frac{1}{C_2} \int_{t_0}^t i(\tau) d\tau + v_2(t_0) \\ &+ \frac{1}{C_3} \int_{t_0}^t i(\tau) d\tau + v_3(t_0) \\ &= \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right) \int_{t_0}^t i(\tau) d\tau \\ &\quad + [v_1(t_0) + v_2(t_0) + v_3(t_0)] \\ &= \frac{1}{C_{eq}} \int_{t_0}^t i(\tau) d\tau + v_{eq}(t_0) \end{aligned}$$

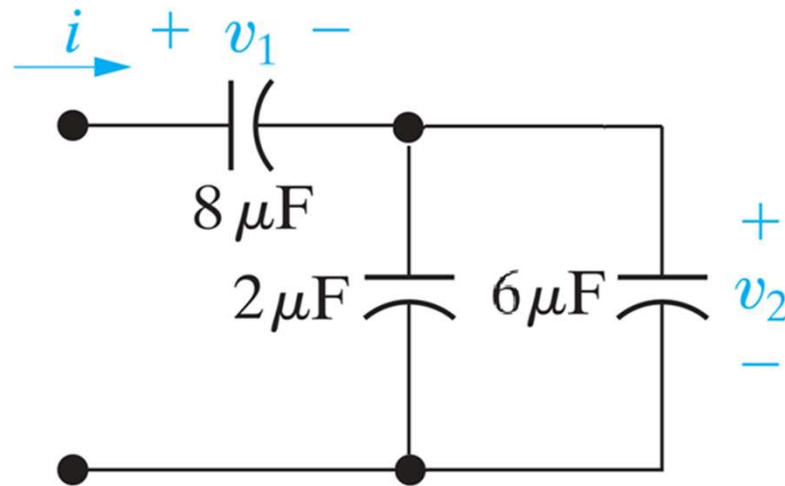**Capacitors combine in series like resistors or inductors combine in parallel.**



Find the equivalent capacitance for the circuit below, assuming  $v_1 = 12\text{ V}$  and  $v_2 = -8\text{ V}$ .



- A.  $C_{\text{eq}} = 4\ \mu\text{F}$ ,  $v_{\text{eq}} = 4\text{ V}$
- B.  $C_{\text{eq}} = 9.5\ \mu\text{F}$ ,  $v_{\text{eq}} = 4\text{ V}$
- C.  $C_{\text{eq}} = 4\ \mu\text{F}$ ,  $v_{\text{eq}} = 20\text{ V}$



# Inductor and Capacitor comparison

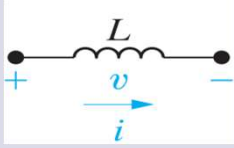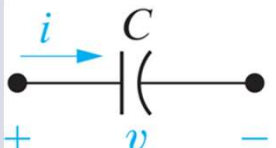	Inductor	Capacitor
<b>Symbol</b>		
<b>Units</b>	Henries [H]	Farads [F]
<b>Describing equation</b>	$v(t) = L \frac{di(t)}{dt}$	$i(t) = C \frac{dv(t)}{dt}$
<b>Other equation</b>	$i(t) = \frac{1}{L} \int_{t_o}^t v(\tau) d\tau + i(t_o)$	$v(t) = \frac{1}{C} \int_{t_o}^t i(\tau) d\tau + v(t_o)$
<b>Initial condition</b>	$i(t_o)$	$v(t_o)$
<b>Behavior with const. source</b>	If $i(t) = I$ , $v(t) = 0$ → short circuit	If $v(t) = V$ , $i(t) = 0$ → open circuit
<b>Continuity requirement</b>	$i(t)$ is continuous so $v(t)$ is finite	$v(t)$ is continuous so $i(t)$ is finite

# Inductor and Capacitor comparison

	<b>Inductor</b>	<b>Capacitor</b>
<b>Power</b>	$p(t) = v(t)i(t) = Li(t)\frac{di(t)}{dt}$	$p(t) = v(t)i(t) = Cv(t)\frac{dv(t)}{dt}$
<b>Energy</b>	$w(t) = \frac{1}{2} Li(t)^2$	$w(t) = \frac{1}{2} Cv(t)^2$
<b>Initial energy</b>	$w_o(t) = \frac{1}{2} Li(t_o)^2$	$w_o(t) = \frac{1}{2} Cv(t_o)^2$
<b>Trapped energy</b>	$w(\infty) = \frac{1}{2} Li(\infty)^2$	$w(\infty) = \frac{1}{2} Cv(\infty)^2$
<b>Series-connected</b>	$L_{eq} = L_1 + L_2 + L_2$ $i_{eq}(t_o) = i(t_o)$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ $v_{eq}(t_o) = v_1(t_o) + v_2(t_o) + v_3(t_o)$
<b>Parallel-connected</b>	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$ $i_{eq}(t_o) = i_1(t_o) + i_2(t_o) + i_3(t_o)$	$C_{eq} = C_1 + C_2 + C_2$ $v_{eq}(t_o) = v(t_o)$