ECE 281 Electrical Circuits and Instrumentation + Laboratory Fall 2016/2017 LAB # 7

14**.11.2016**

Objective:

- 1. To study R/2R ladder network
- 2. Find the internal resistance of a battery cell.

1. To study R/2R ladder network (50 Points)

Procedure:

- 1. Construct the ladder circuit shown in Figure 1 with three input nodes.
- 2. Use a digital multi-meter to measure voltages and resistances.



Figure 1

- **3.** When switch is "ON" connect A, B and C to 10V. When switch is "OFF" connect points to the ground.
- **4.** Construct the Table 1 by filling the voltage values for the given switch position combinations.

Switch 1 (SW1)	Switch 2 (SW2)	Switch 3 (SW1)	Voltage	
OFF	OFF	OFF		
OFF	OFF	ON		
OFF	ON	OFF		
OFF	ON	ON		
ON	OFF	OFF		
ON	OFF	ON		
ON	ON	OFF		
ON	ON	ON		

Table 1

- 5. Now, remove the power supply and construct the Table 2.
- 6. "ON" do not connect node to anywhere. "OFF" connect node to the ground.

Switch 1 (SW1)	Switch 2 (SW2)	Switch 3 (SW1)	Resistance
OFF	OFF	OFF	
OFF	OFF	ON	
OFF	ON	OFF	
OFF	ON	ON	
ON	OFF	OFF	
ON	OFF	ON	
ON	ON	OFF	
ON	ON	ON	

7. Check the following values

Lowest voltage $\cong 0$

Highest Voltage = $\frac{2^{N} - 1}{2^{N}}$. V_{source} N = number of switch points

2. Find the internal resistance(R_s) of a battery cell.(50 Points)

Procedure:

1. Construct the circuit shown in Figure 2.



Figure 2

- 2. Use a digital multi-meter to measure voltages and currents.
- 3. With the switch (SW1) "OPEN" measure voltage between point A and ground (E).
- 4. "CLOSE" switch, again measure voltage between point A and ground (V_L).
- 5. Measure current between A-B(I_L).
- 6. Calculate the internal resistance of a battery cell (R_s)
- 7. Construct Table 3. Draw the theoretically correct circuit. By replacing E with V_L and R_s .

Voltage with SW1 OPEN			<u>Circuit Box</u>
Voltage with SW1 is CLOSE			
Current out of the cell	IL		
$\frac{\text{Calculation Box}}{R_s = \frac{E - V_L}{I_L}}$			