




Response of First-Order RL/RC Circuits

Objectives:

- Natural response of RL/RC circuits
- Step response of RL/RC circuits
- Sequential switching in first-order circuits


RL Natural Response

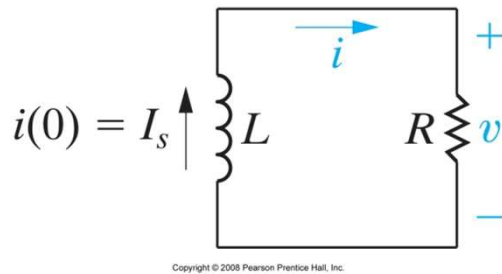

The problem: Given an initial current $i(0)$ through L at $t = 0$, find $i(t)$ for $t \geq 0$.

Note: this is the “natural” response of this circuit because for $t \geq 0$ there is no independent source in the circuit – the response is due only to the “nature” of the components and their interconnection.

RL Natural Response

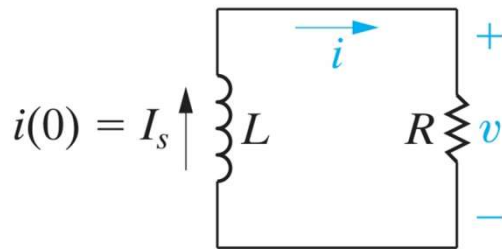

Copyright © 2008 Pearson Prentice Hall, Inc.




$$\text{KVL: } L \frac{di(t)}{dt} + Ri(t) = 0$$

This equation is a


- First-order (the highest derivative is a first derivative)
- Homogeneous (the right-hand side is 0)
- Ordinary differential equation
- With constant coefficients

The solution to the differential equation, repeated below, must be a function whose first-derivative has the same form as the function. Which one of these functions exhibits this behavior?

$$\text{KVL: } L \frac{di(t)}{dt} + Ri(t) = 0$$

-  A. $K \sin \omega t$
-  B. Ke^{-at}
-  C. Kt^2

RL Natural Response

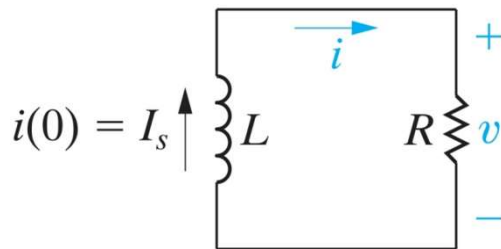

$$\text{KVL: } L \frac{di(t)}{dt} + Ri(t) = 0$$

$$\text{Let } i(t) = e^{-at} \quad \text{and} \quad \frac{di(t)}{dt} = -ae^{-at}$$

$$\text{Substituting, } L(-ae^{-at}) + Re^{-at} = 0$$


$$\text{Rearranging, } (R - aL)e^{-at} = 0 \quad \text{so} \quad R - aL = 0$$

$$\text{Solving, } a = R/L$$

$$\text{But } i(0) = I_s \quad \text{so} \quad i(t) = I_s e^{-(R/L)t}, \quad t \geq 0$$

$$\begin{aligned} \text{Check: } & L(-R/L)I_s e^{-(R/L)t} + RI_s e^{-(R/L)t} \\ &= -RI_s e^{-(R/L)t} + RI_s e^{-(R/L)t} = 0 \end{aligned}$$


$$i(0) = I_s e^{-(R/L)(0)} = I_s$$

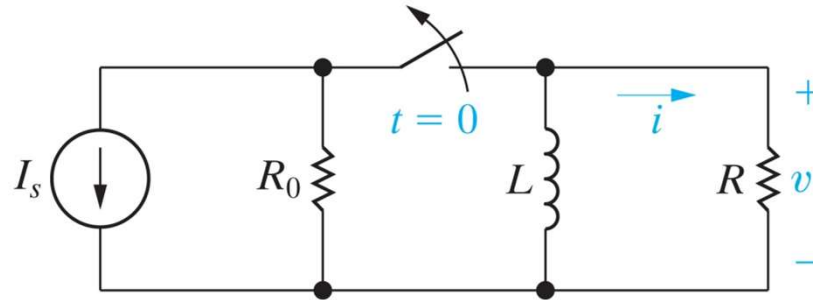

Copyright © 2008 Pearson Prentice Hall, Inc.

Here is one circuit that can be used to establish the initial current through the inductor. For $t < 0$, the inductor can be replaced by

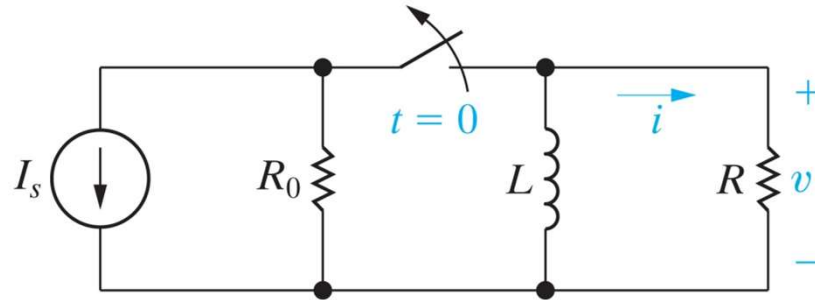- X** A. An open circuit
- ✓** B. A short circuit
- X** C. A resistor




Copyright © 2008 Pearson Prentice Hall, Inc.

To evaluate the current in the inductor for $t < 0$, close the switch and replace the inductor with a short circuit. The current from bottom to top in the short circuit is


- X** A. $-I_s$
- X** B. $RI_s / (R + R_0)$
- ✓** C. I_s

RL Natural Response

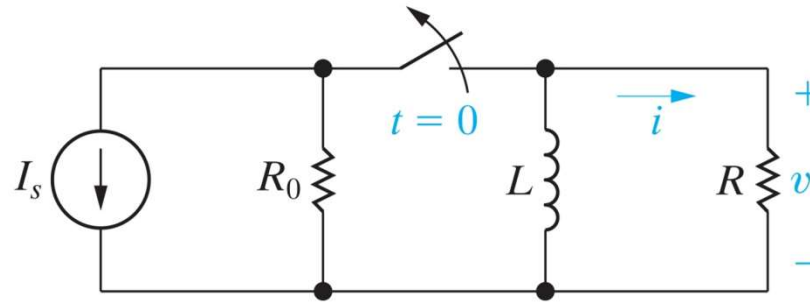


Copyright © 2008 Pearson Prentice Hall, Inc.

$t < 0$:

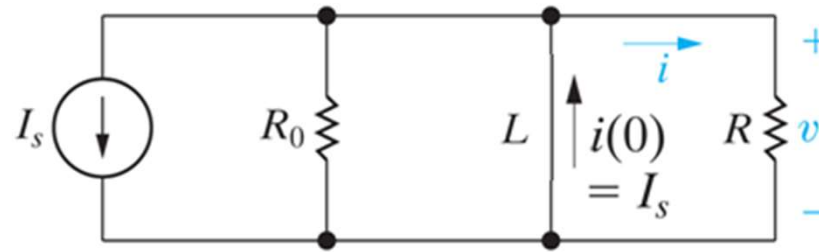


$t \geq 0$:

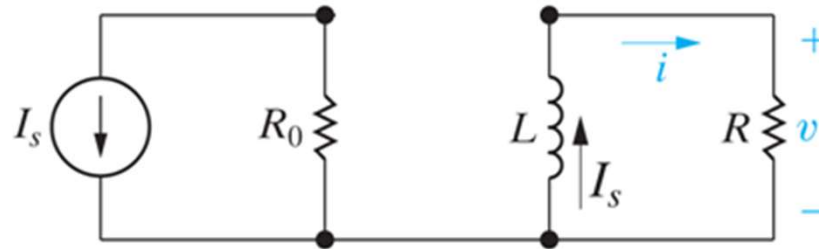


$$i(t) = I_s e^{-(R/L)t}, \quad t \geq 0$$

RC Natural Response

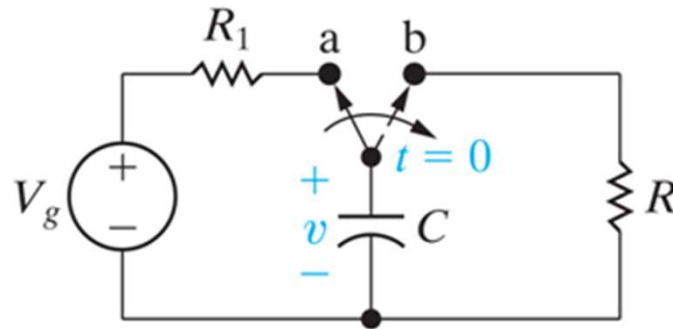


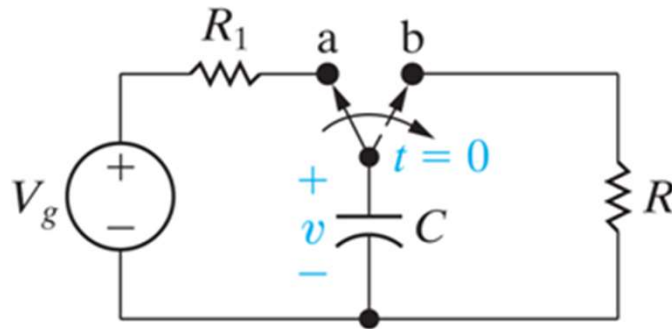The problem: Find $v(t)$ for $t \geq 0$. Note that the circuit to the left of the capacitor establishes an initial voltage drop $v(0)$ across C at $t = 0$.



Here is the circuit for the RC natural response problem. For $t < 0$, the capacitor can be replaced by

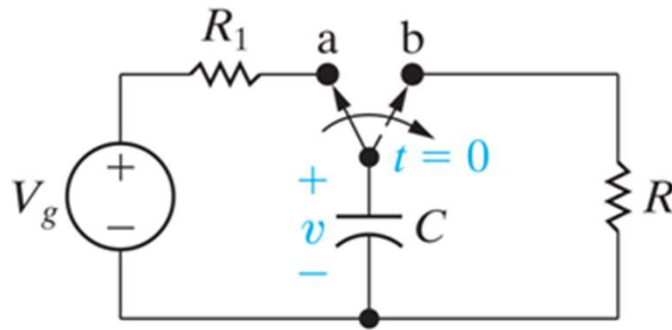- A. An open circuit
- B. A short circuit
- C. A constant current




To evaluate the voltage drop across the capacitor for $t < 0$, put the switch in the “a” position and replace the capacitor with an open circuit. The voltage drop across the open circuit, positive at the top, is

- ✓ A. V_g
- ✗ B. $-V_g$
- ✗ C. $RV_g / (R + R_1)$

RC Natural Response

$t < 0$:

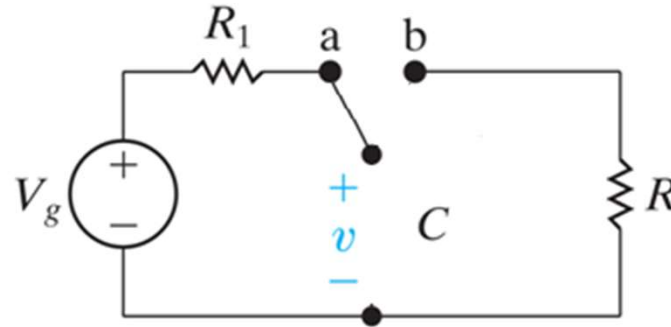

There is an open circuit here, so the current in this circuit is 0, and the voltage drop across R_1 is 0. Thus,


$$v = V_g, \quad t < 0$$

Remember the continuity requirement for capacitors – the voltage drop across the capacitor must be continuous everywhere, so that the current through the capacitor remains finite. Thus,

$$v(0) = V_g$$

RC Natural Response

$t \geq 0$:

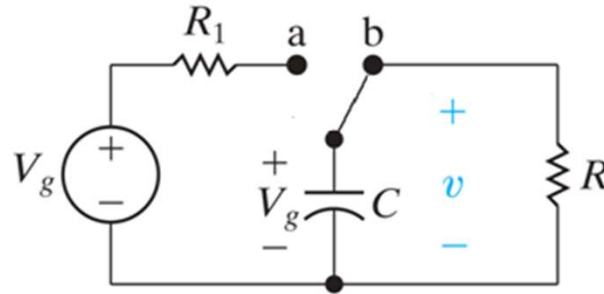

$$\text{KCL: } C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0$$

$$\text{Let } v(t) = e^{-at} \quad \text{and} \quad \frac{dv(t)}{dt} = -ae^{-at}$$


$$\text{Substituting, } C(-ae^{-at}) + e^{-at}/R = 0$$

$$\text{Rearranging, } (1/R - aC)e^{-at} = 0 \quad \text{so} \quad 1/R - aC = 0$$


$$\text{Solving, } a = 1/RC$$

$$\text{But } v(0) = V_g \quad \text{so} \quad v(t) = V_g e^{-(1/RC)t}, \quad t \geq 0$$

RL/RC Natural Response

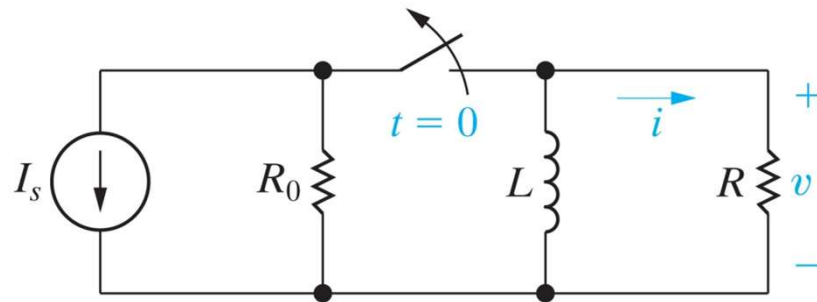

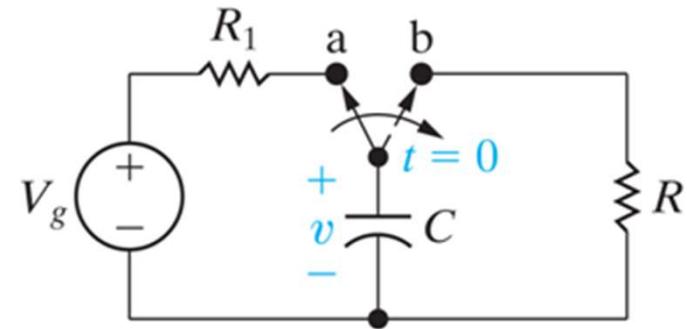Copyright © 2008 Pearson Prentice Hall, Inc.



$$\text{KVL: } L \frac{di(t)}{dt} + Ri(t) = 0$$

$$i(0) = I_s$$

$$i(t) = I_s e^{-(R/L)t}, \quad t \geq 0$$

$$\text{KCL: } C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0$$

$$v(0) = V_g$$

$$v(t) = V_g e^{-(1/RC)t}, \quad t \geq 0$$

The form of the natural response is the same:




$$ICe^{-t/\tau}$$

IC is the initial condition and τ is the **time constant**, a measure of how quickly or slowly the exponential decays.

The form of the RL/RC natural response is

$$I C e^{-t/\tau}$$




The units for the time constant, τ , must be

-  A. s (seconds)
-  B. s^{-1} (inverse seconds)
-  C. τ has no units

The RL natural response is

$$i(t) = I_s e^{-(R/L)t}, \quad t \geq 0$$

Therefore, the time constant, τ , for the RL circuit is

-  A. R/L
-  B. L/Rt
-  C. L/R

RL/RC Natural Response

A general solution method:

1. Identify the variable of interest (hint – it's the variable that must be continuous in the circuit):
 - For RL, $i(t)$ through L
 - For RC, $v(t)$ across C
2. Find the initial value of this variable, either $i(0) = I_0$ or $v(0) = V_0$
 - From the problem statement
 - By analyzing the circuit for $t < 0$, with L replaced by a short circuit or C replaced by an open circuit
3. Find the time constant, τ
 - $\tau_{RL} = L/R_{eq}$ or $\tau_{RC} = R_{eq}C$
 - Note that R_{eq} is the equivalent resistance as seen from the inductor or capacitor for $t \geq 0$

RL/RC Natural Response

A general solution method, continued:

4. Write the expression for the variable of interest:

$$x(t) = X_0 e^{-t/\tau}, \quad t \geq 0$$

5. Use simple circuit analysis to calculate any other requested variables.