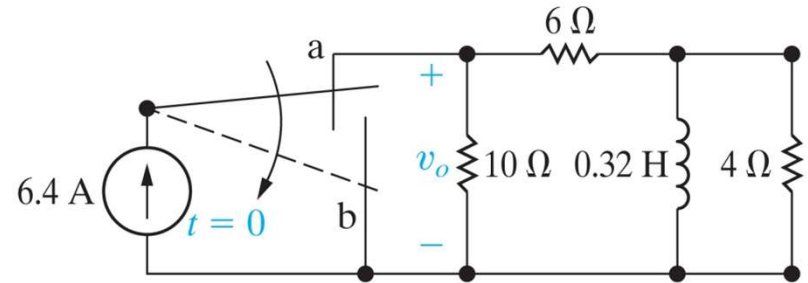


RL/RC Natural Response Summary

1. Identify the variable of interest.
 - For RL, $i(t)$ through L; For RC, $v(t)$ across C
2. Find the initial value of this variable, either $i(0) = I_0$ or $v(0) = V_0$. Usually, analyze the circuit for $t < 0$.
3. Find the time constant, τ
 - $\tau_{RL} = L/R_{eq}$ or $\tau_{RC} = R_{eq}C$
 - R_{eq} is the equivalent resistance seen by the inductor or capacitor.
4. Write the expression for the variable of interest:
$$x(t) = X_0 e^{-t/\tau}, \quad t \geq 0.$$
5. Use simple circuit analysis to calculate any other requested variables.

RL/RC Natural Response Examples


AP 7.2 – Find $v_o(t)$ for $t \geq 0^+$




Copyright © 2008 Pearson Prentice Hall, Inc.

1. Variable of interest is the current through the inductor, so mark it on the circuit.
2. Find the initial current in the inductor:

For $t < 0$

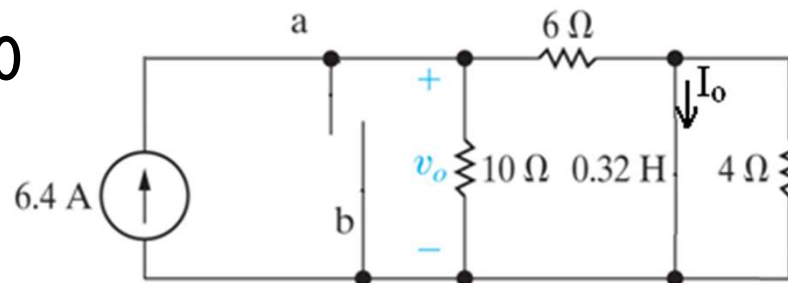


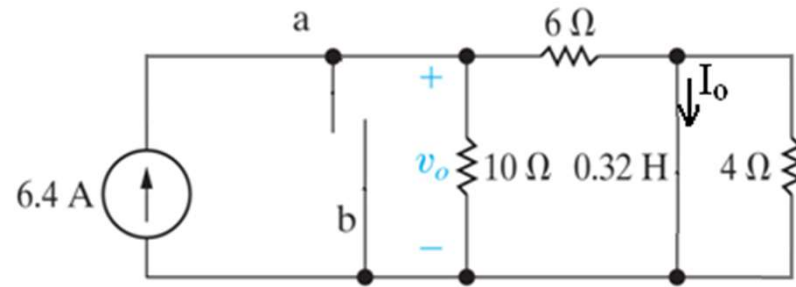The short circuit that replaced the inductor effectively eliminates which resistor from this circuit?



- X** A. 10 Ω
- X** B. 6 Ω
- ✓** C. 4 Ω

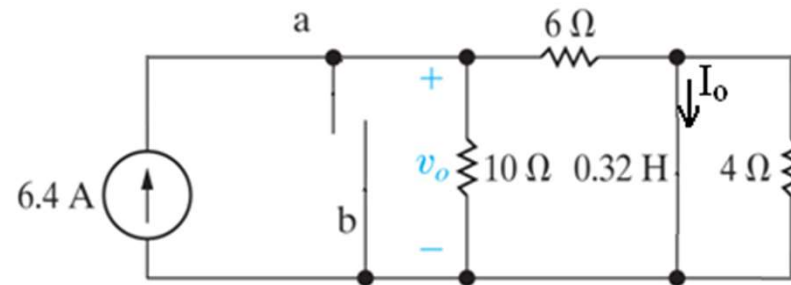
What circuit analysis tool provides the most direct method to calculate I_o ?



- X** A. Node voltage method
- ✓** B. Current division
- X** C. Source transformation

RL/RC Natural Response Examples


AP 7.2 – Find $v_o(t)$ for $t \geq 0^+$

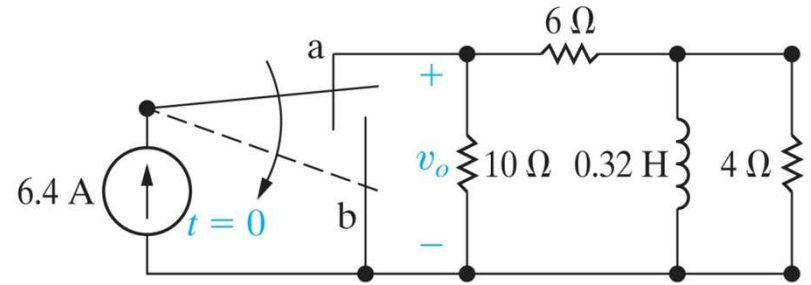

Copyright © 2008 Pearson Prentice Hall, Inc.

2. Find the initial current in the inductor:


For $t < 0$

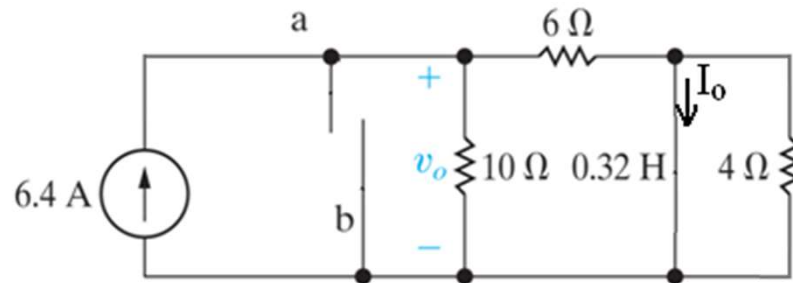

Current division:
$$I_o = \frac{10}{10 + 6} (6.4) = 4 \text{ A}$$

RL/RC Natural Response Examples


AP 7.2 – Find $v_o(t)$ for $t \geq 0^+$

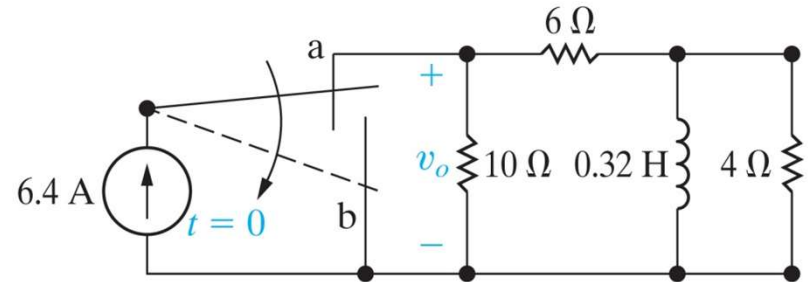


Copyright © 2008 Pearson Prentice Hall, Inc.

3. Find the time constant, $\tau = L/R_{eq}$:


For $t \geq 0$

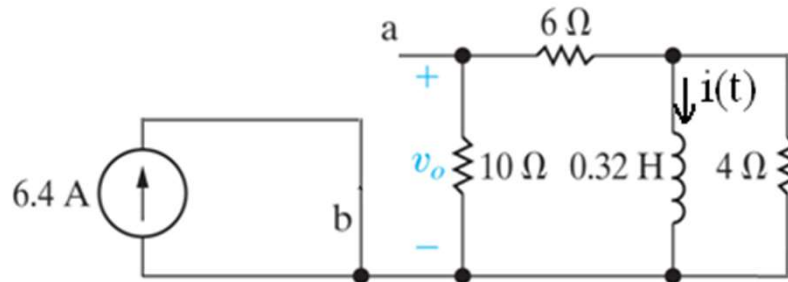

Simplified:

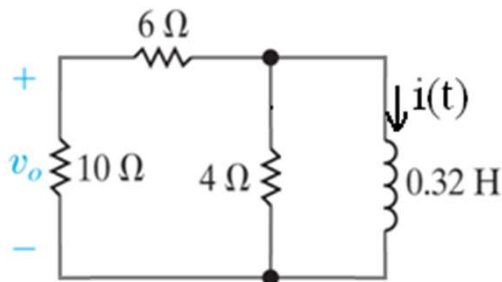

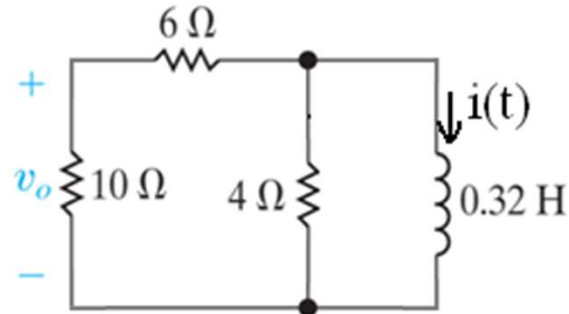
The expression for the equivalent resistance seen by the inductor is



- A. $4 \parallel (10 + 6)$
- B. $10 \parallel (6 + 4)$
- C. $10 + 6 + 4$

RL/RC Natural Response Examples


AP 7.2 – Find $v_o(t)$ for $t \geq 0^+$

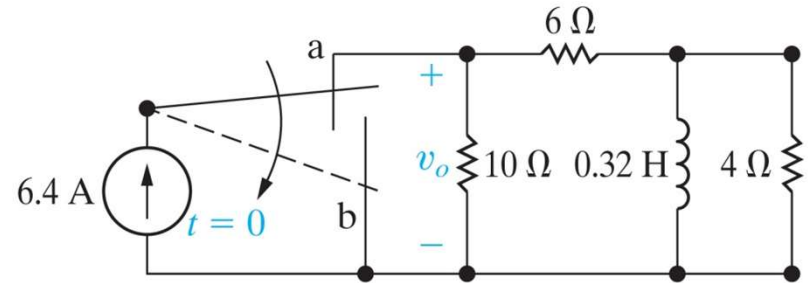

Copyright © 2008 Pearson Prentice Hall, Inc.

3. Find the time constant, $\tau = L/R_{eq}$:

For $t \geq 0$

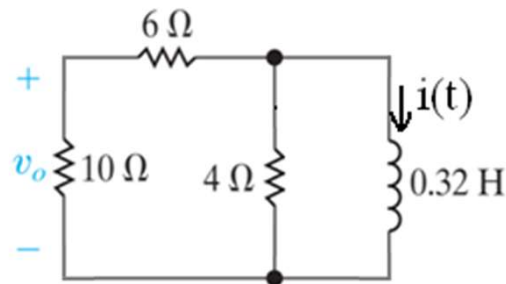

$$R_{eq} = 4 \parallel (6 + 10) = 3.2 \Omega$$

$$\tau = L / R_{eq} = 0.32 / 3.2 = 0.1 \text{ s}$$

4. $i(t) = ICe^{-t/\tau} = 4e^{-t/0.1} = 4e^{-10t} \text{ A}, t \geq 0$


5. Find $v_o(t)$:

$$v_L(t) = (0.32) \frac{d}{dt} (4e^{-10t}) = (0.32)(-10)(4e^{-10t})$$

$$= -12.8e^{-10t} \text{ V}, t \geq 0^+$$


$$v_o(t) = \frac{10}{10+6} v_L(t) = -8e^{-10t} \text{ V}, t \geq 0^+$$

In circuits with inductors, we solve for the inductor current and the solution is valid for $t \geq 0$. When we use the inductor current to solve for any other voltage or current in the circuit, the resulting expression is valid for $t \geq 0^+$ because none of these other quantities are required to be continuous everywhere.

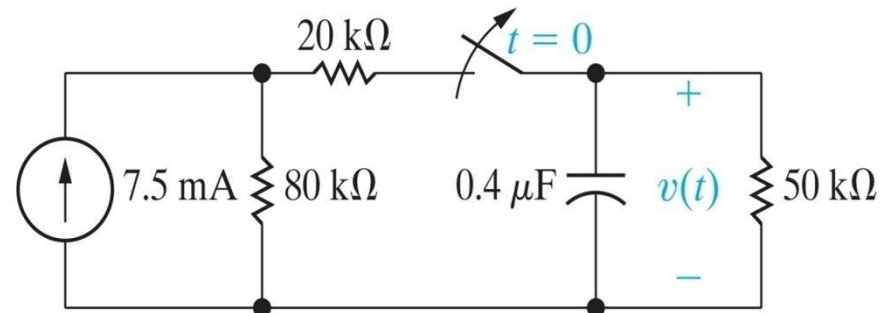-  A. True
-  B. False

RL/RC Natural Response Examples


AP 7.3 – Find the time at which 75% of the initial stored energy has been dissipated.




Copyright © 2008 Pearson Prentice Hall, Inc.

1. Variable of interest is the voltage drop across the capacitor, which is already marked on the circuit.
2. Find the initial voltage drop across the capacitor:

$t < 0$:

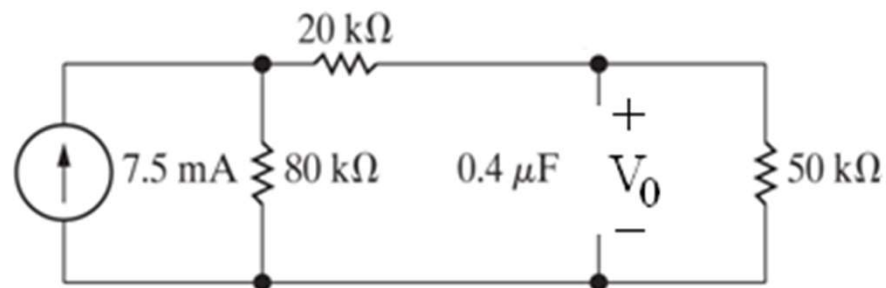

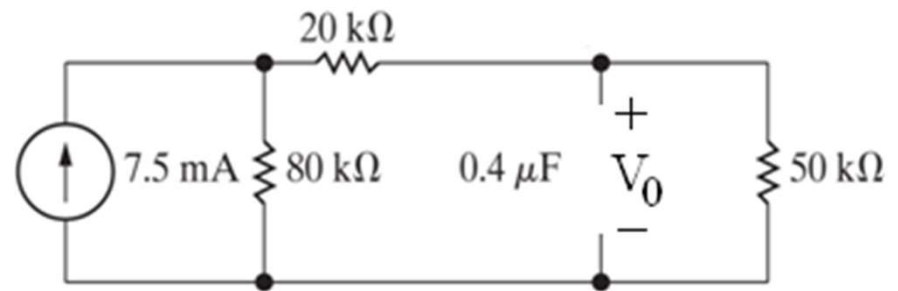
In the circuit used to find the initial voltage drop across the capacitor, the voltage drop across the open circuit is the same as the voltage drop across



- X** A. The 80 kΩ resistor
- ✓** B. The 50 kΩ resistor
- X** C. The 20 kΩ resistor



RL/RC Natural Response Examples

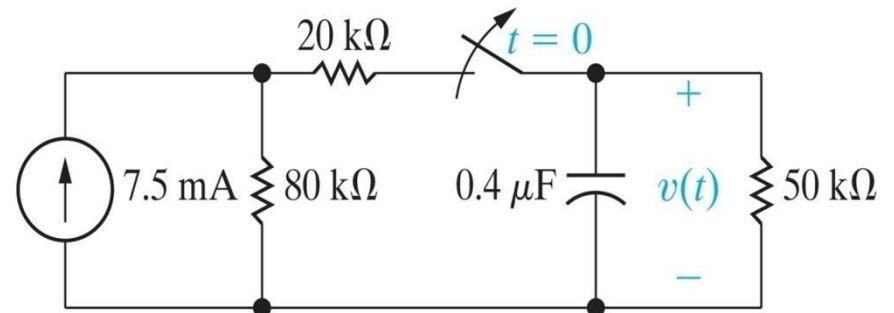AP 7.3 – Find the time at which 75% of the initial stored energy has been dissipated.



Copyright © 2008 Pearson Prentice Hall, Inc.

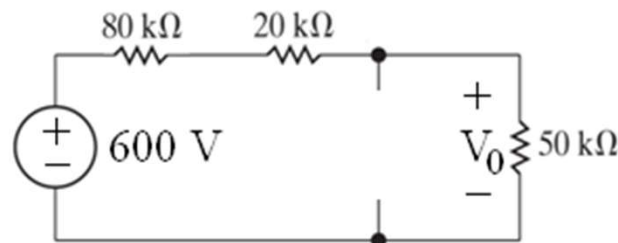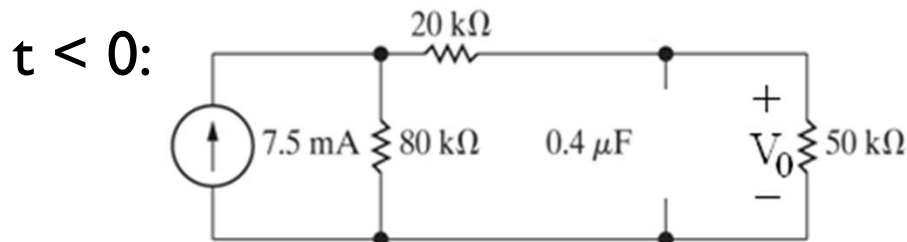
2. Find the initial voltage drop across the capacitor:



$$V_0 = \frac{50 \text{ k}}{80 \text{ k} + 20 \text{ k} + 50 \text{ k}} (600) = 200 \text{ V}$$

RL/RC Natural Response Examples

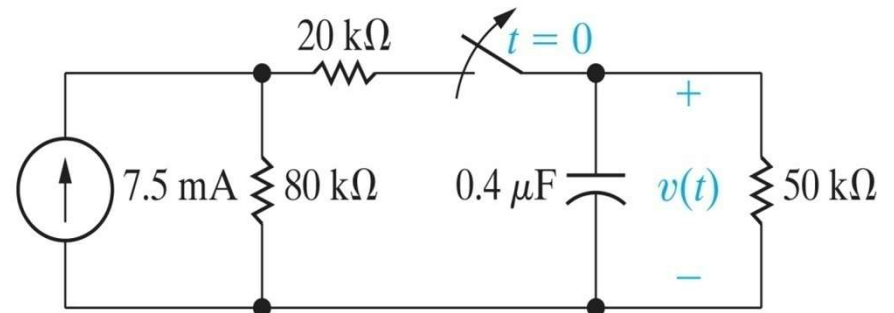AP 7.3 – Find the time at which 75% of the initial stored energy has been dissipated.



Copyright © 2008 Pearson Prentice Hall, Inc.

3. Find the time constant, $\tau = R_{eq} C$


$t \geq 0$:

$\tau = (50,000)(0.4 \times 10^{-6}) = 0.02 \text{ s}$

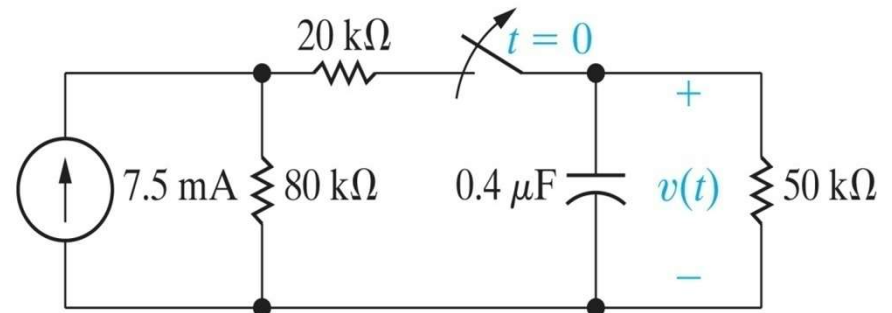
4. $v(t) = ICe^{-t/\tau} = 200e^{-t/0.02} = 200e^{-50t} \text{ V}, t \geq 0$

RL/RC Natural Response Examples

AP 7.3 – Find the time at which 75% of the initial stored energy has been dissipated.



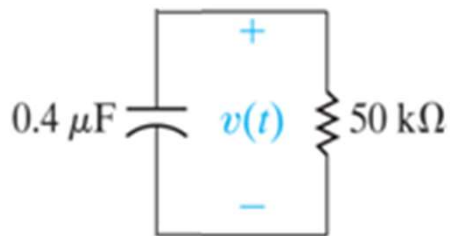Copyright © 2008 Pearson Prentice Hall, Inc.



$$v(t) = 200e^{-50t} \text{ V}, \quad t \geq 0$$

5. Find the initial energy. $w(0) = \frac{1}{2}(0.4 \times 10^{-6})(200)^2 = 8 \text{ mJ}$

75% of the initial energy is 6 mJ, so the energy that remains is 2 mJ. Thus,

$$w(t) = \frac{1}{2}(0.4 \times 10^{-6})(200e^{-50t})^2 = 8e^{-100t} \text{ mJ} = 2 \text{ mJ}$$

$$\Rightarrow e^{-100t} = 0.25 \quad \Rightarrow t = \frac{\ln(0.25)}{-100} = 13.86 \text{ ms}$$