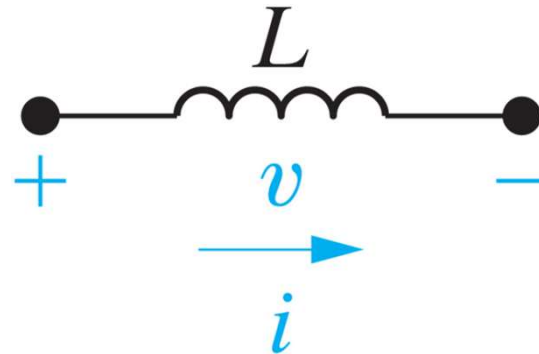


Chapter 6 - Inductance and Capacitance

- Objectives:
 - Inductor
 - Equations for v , i , p , and w
 - Behavior in the presence of constant current
 - Continuity requirements
 - Combine in series and in parallel
 - Capacitor
 - Equations for v , i , p , and w
 - Behavior in the presence of constant voltage
 - Continuity requirements
 - Combine in series and in parallel

Inductor



- Coil of wire with time-varying current
 - time-varying magnetic field
 - time-varying voltage drop

- Inductor equation:
$$v(t) = L \frac{di(t)}{dt}$$

- Units: $v(t)$ is volts, $i(t)$ is amps, and L is henries [H]




Look at the inductor equation again:

$$v(t) = L \frac{di(t)}{dt}$$

Suppose $i(t)$ is constant. Then $v(t) =$

- X** A. L
- ✓** B. 0
- X** C. Undefined

So, if the current in an inductor is constant, its voltage drop is 0, so the inductor can be replaced by

-  A. A short circuit
-  B. An open circuit
-  C. A capacitor

Inductor

- **If the current in the inductor is constant, the voltage is 0, so the inductor can be replaced by a SHORT CIRCUIT.**

- Look at the inductor equation again: $v(t) = L \frac{di(t)}{dt}$

- Suppose there is a discontinuity in $i(t)$ – that is, at some value of t , the current jumps instantaneously. At this value of t , the derivative of the current is infinite. Therefore the voltage is infinite! NOT POSSIBLE.

- **Thus, the current through an inductor is continuous for all time.**

We just showed that the current in an inductor must be continuous for all time. This means that the voltage must also be continuous for all time.

-  A. True
-  B. False

Inductor

- The equation for current in terms of voltage:

$$v(t) = L \frac{di(t)}{dt} \quad \Rightarrow \quad v(t)dt = Ldi(t)$$

$$\Rightarrow \int_{t_o}^t v(\tau)d\tau = L \int_{i(t_o)}^{i(t)} dx$$

$$\Rightarrow i(t) = \frac{1}{L} \int_{t_o}^t v(\tau)d\tau + i(t_o)$$

Inductor

- Power and energy

$$p(t) = v(t)i(t) = Li(t)\frac{di(t)}{dt} \quad (\text{passive sign convention!})$$

$$p(t) = \frac{dw(t)}{dt} = Li(t)\frac{di(t)}{dt}$$

$$\Rightarrow dw(\tau) = Li(\tau)di(\tau)$$




$$\Rightarrow \int_0^{w(t)} dx = L \int_0^{i(t)} y(\tau)d\tau$$

$$\Rightarrow w(t) = \frac{1}{2} Li(t)^2$$

Inductor


- Inductors are **energy storage devices!**
 - If the initial current through the inductor is non-zero, the inductor is storing energy.

Suppose the initial current through a 2 mH inductor is 1 A. The initial energy stored in the inductor is

-  A. 1 mJ
-  B. 2 mJ
-  C. 4 mJ

Inductor

- Example – Assessment Problem 6.1

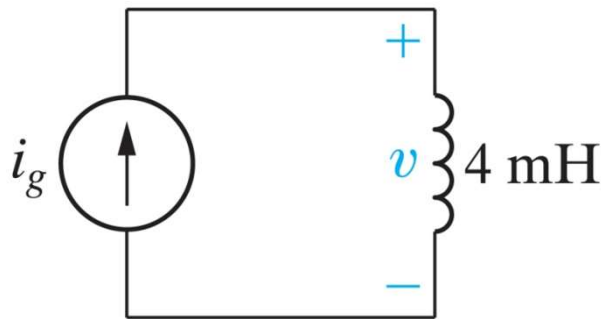

$$i_g(t) = 0, \quad t < 0,$$

$$i_g(t) = 8e^{-300t} - 8e^{-1200t} \text{ A}, \quad t \geq 0.$$

Is the current continuous? $i(0) = 8 - 8 = 0$: YES!

Find the voltage:

$$v(t) = 0, \quad t < 0$$


$$v(t) = L \frac{di(t)}{dt} = (0.004)[(-300)8e^{-300t} - (-1200)8e^{-1200t}]$$

$$= -9.6e^{-300t} + 38.4e^{-1200t} \text{ V}, \quad t \geq 0$$

Is the voltage continuous? $v(0) = -9.6 + 38.4 = 28.8 \text{ V}$:
NO!

Inductor

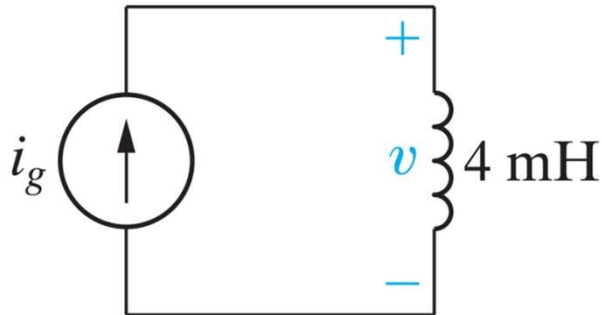- Example – Assessment Problem 6.1, continued



Copyright © 2008 Pearson Prentice Hall, Inc.

$$i_g(t) = 0, \quad t < 0,$$
$$i_g(t) = 8e^{-300t} - 8e^{-1200t} \text{ A}, \quad t \geq 0.$$


Find the power for the inductor:

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= (-9.6e^{-300t} + 38.4e^{-1200t})(8e^{-300t} - 8e^{-1200t}) \\ &= -76.8e^{-600t} + 384e^{-1500t} - 307.2e^{-2400t} \text{ W} \end{aligned}$$

To find the max power and the time at which the power is max, take the first derivative of $p(t)$ and set it equal to 0.

Inductor

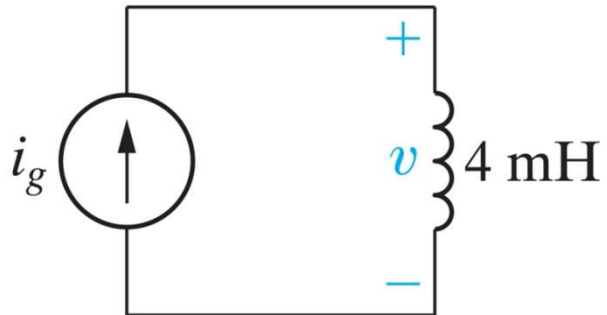- Example – Assessment Problem 6.1, continued



Copyright © 2008 Pearson Prentice Hall, Inc.

$$i_g(t) = 0, \quad t < 0,$$


$$i_g(t) = 8e^{-300t} - 8e^{-1200t} \text{ A}, \quad t \geq 0.$$

Find the energy for the inductor:

$$\begin{aligned} w(t) &= \frac{1}{2} Li(t)^2 \\ &= \frac{1}{2} (0.004)(8e^{-300t} - 8e^{-1200t})^2 \\ &= 128(e^{-600t} - 2e^{-1500t} + e^{-2400t}) \text{ mJ} \end{aligned}$$

To find the max energy and the time at which the energy is max, take the first derivative of $w(t)$ and set it equal to 0. Or if you don't have $w(t)$ yet, do the same for $i(t)$!

Inductors in series and parallel

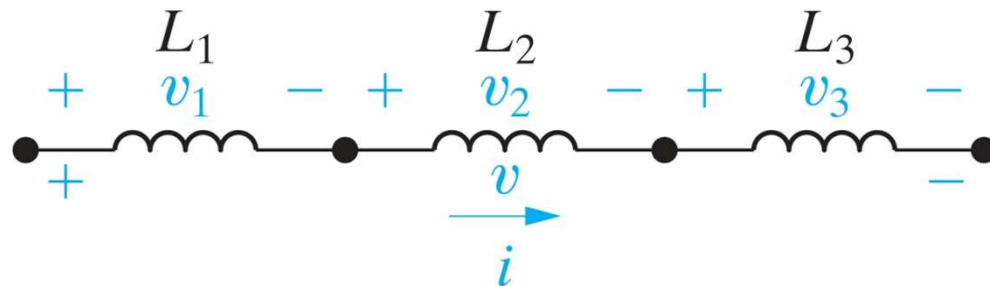


Copyright © 2008 Pearson Prentice Hall, Inc.

$$v_1 = L_1 \frac{di}{dt}, \quad v_2 = L_2 \frac{di}{dt}, \quad \text{and} \quad v_3 = L_3 \frac{di}{dt}.$$

KVL:
$$v = v_1 + v_2 + v_3 = (L_1 + L_2 + L_3) \frac{di}{dt},$$

Inductors in series ADD.

Inductors in series and parallel

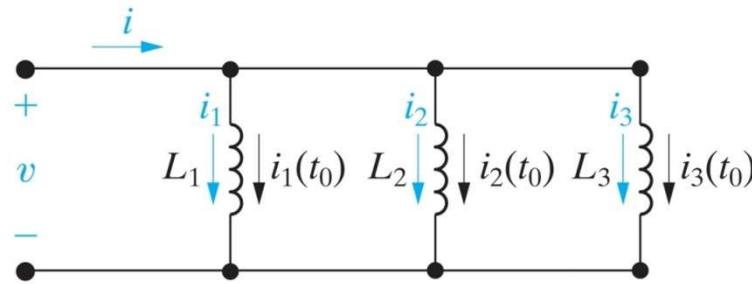

Copyright © 2008 Pearson Prentice Hall, Inc.

$$i_1 = \frac{1}{L_1} \int_{t_0}^t v d\tau + i_1(t_0), \quad i_2 = \frac{1}{L_2} \int_{t_0}^t v d\tau + i_2(t_0), \quad i_3 = \frac{1}{L_3} \int_{t_0}^t v d\tau + i_3(t_0).$$

$$\text{KCL:} \quad i = i_1 + i_2 + i_3.$$

$$i = \left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right) \int_{t_0}^t v d\tau + i_1(t_0) + i_2(t_0) + i_3(t_0).$$


$$i = \frac{1}{L_{\text{eq}}} \int_{t_0}^t v d\tau + i(t_0).$$

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

Inductors combine in parallel like resistors combine in parallel.


$$i(t_0) = i_1(t_0) + i_2(t_0) + i_3(t_0).$$

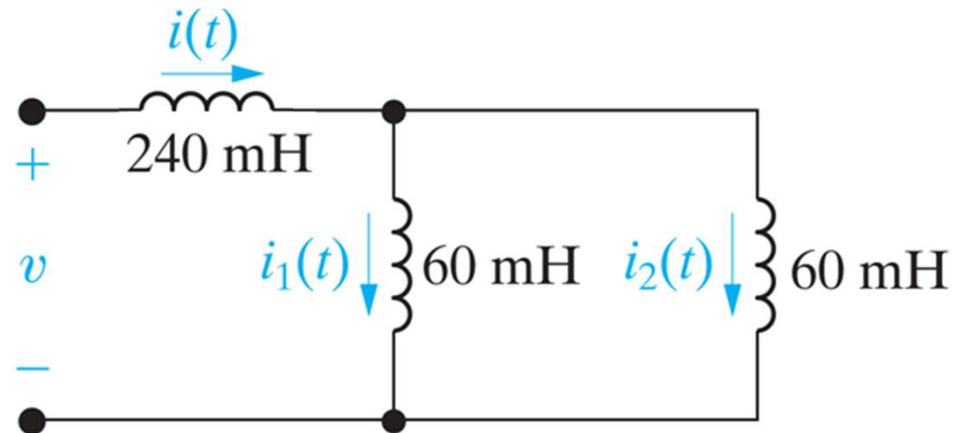Find the equivalent inductance for the circuit below, assuming $i_1 = 6 \text{ A}$ and $i_2 = -3 \text{ A}$.



- X** A. $L_{\text{eq}} = 300 \text{ mH}$, $i(t) = 6 \text{ A}$
- X** B. $L_{\text{eq}} = 270 \text{ mH}$, $i(t) = -3 \text{ A}$
- ✓** C. $L_{\text{eq}} = 270 \text{ mH}$, $i(t) = 3 \text{ A}$

Inductor summary
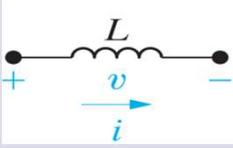
| | |
|------------------------------------|--|
| Symbol |  <p>The diagram shows a horizontal wire with a wavy line representing an inductor. Above the wire is the letter 'L'. Below the wire, a blue arrow labeled 'v' points to the right, and a blue arrow labeled 'i' points to the right. The left end of the wire has a '+' sign, and the right end has a '-' sign.</p> |
| Units | Henries [H] |
| Describing equation | $v(t) = L \frac{di(t)}{dt}$ |
| Other equation | $i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$ |
| Initial condition | $i(t_0)$ |
| Behavior with const. source | If $i(t) = I$, $v(t) = 0 \rightarrow$ short circuit |
| Continuity requirement | $i(t)$ is continuous so $v(t)$ is finite |

Inductor summary

| | |
|---------------------------|--|
| Power | $p(t) = v(t)i(t) = Li(t)\frac{di(t)}{dt}$ |
| Energy | $w(t) = \frac{1}{2}Li(t)^2$ |
| Initial energy | $w_o(t) = \frac{1}{2}Li(t_o)^2$ |
| Trapped energy | $w(\infty) = \frac{1}{2}Li(\infty)^2$ |
| Series-connected | $L_{eq} = L_1 + L_2 + L_2$ $i_{eq}(t_o) = i(t_o)$ |
| Parallel-connected | $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$ $i_{eq}(t_o) = i_1(t_o) + i_2(t_o) + i_3(t_o)$ |