

# **Basic Laws of Electric Circuits**

**Ohms Law**

**Kirchhoff's Current Law**




# Basic Laws of Circuits

---
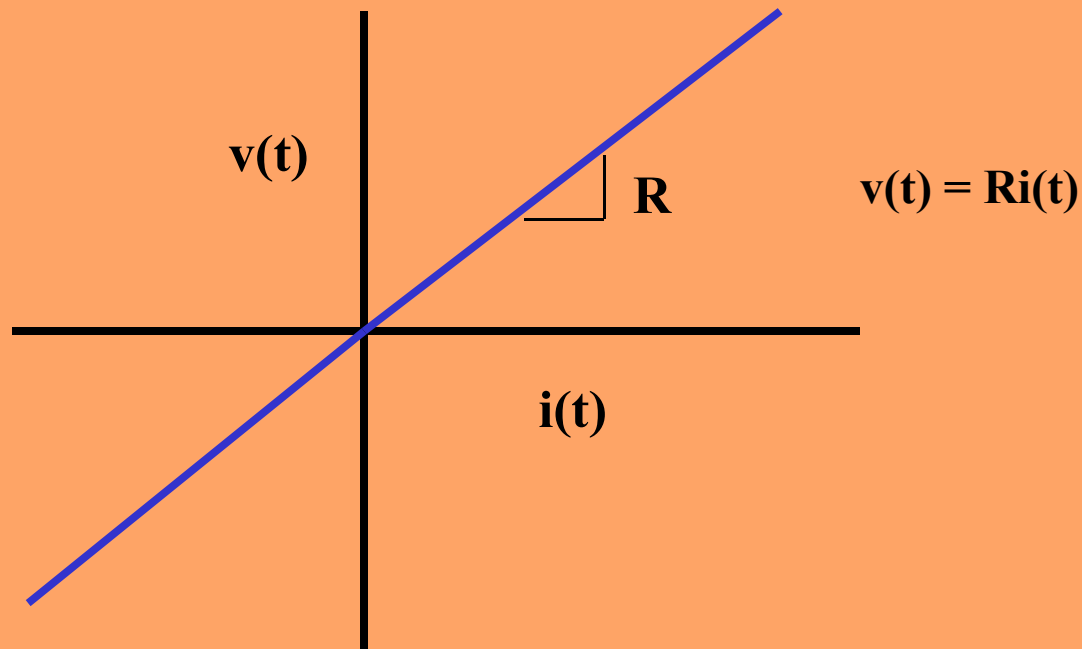
## Ohm's Law:

Directly proportional means a straight line relationship.



The resistor is a model and will not produce a straight line for all conditions of operation.

# **Basic Laws of Circuits**

---

## **Ohm's Law: About Resistors:**

**The unit of resistance is ohms(  $\Omega$ ).**

**A mathematical expression for resistance is**

$$R = \rho \frac{l}{A} \quad (2.3)$$

*l : The length of the conductor (meters)*

*A : The cross – sectional area (meters<sup>2</sup>)*

*$\rho$  : The resistivity ( $\Omega \cdot m$ )*

# **Basic Laws of Circuits**

---

## **Ohm's Law: About Resistors:**

**We remember that resistance has units of ohms. The reciprocal of resistance is conductance. At one time, conductance commonly had units of mhos (resistance spelled backwards).**

**In recent years the units of conductance has been established as seimans (S).**

**Thus, we express the relationship between conductance and resistance as**

$$G = \frac{1}{R} \quad (\text{S}) \quad (2.4)$$


**We will see later than when resistors are in parallel, it is convenient to use Equation (2.4) to calculate the equivalent resistance.**

# Basic Laws of Circuits

---

## Ohm's Law: Ohm's Law: Example 2.1.

Consider the following circuit.

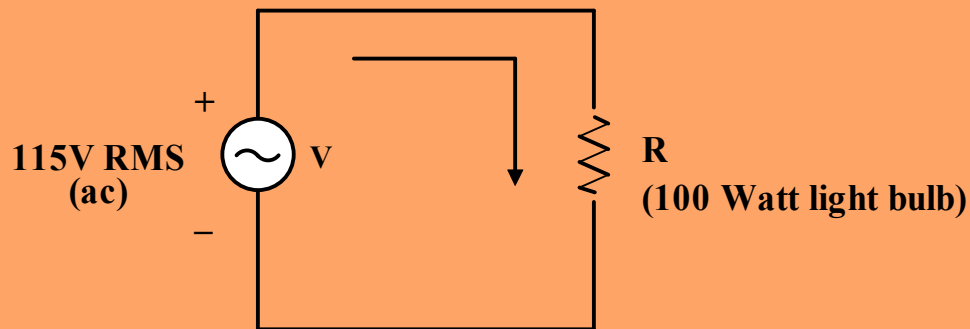

Determine the resistance of the 100 Watt bulb.

$$P = VI = \frac{V^2}{R} = I^2 R \quad (2.5)$$

$$R = \frac{V^2}{P} = \frac{115^2}{100} = 132.25 \text{ ohms}$$

A suggested assignment is to measure the resistance of a 100 watt light bulb with an ohmmeter.

# Basic Laws of Circuits

---

## Ohm's Law: Property of Resistance:

### Resistivities of some basic materials


Material	Resistivity (ohm meters)	Common Use
silver	$1.6 \times 10^{-8}$	conductor
copper	$1.7 \times 10^{-8}$	conductor
aluminum	$2.8 \times 10^{-8}$	conductor
gold	$2.5 \times 10^{-8}$	conductor
carbon	$4.1 \times 10^{-5}$	semiconductor
germanium	$47 \times 10^{-2}$	semiconductor
silicon	$6.4 \times 10^2$	semiconductor
paper	$1 \times 10^{10}$	insulator
mica	$5 \times 10^{11}$	insulator
glass	$1 \times 10^{12}$	insulator
teflon	$3 \times 10^{12}$	insulator

# Basic Laws of Circuits

---
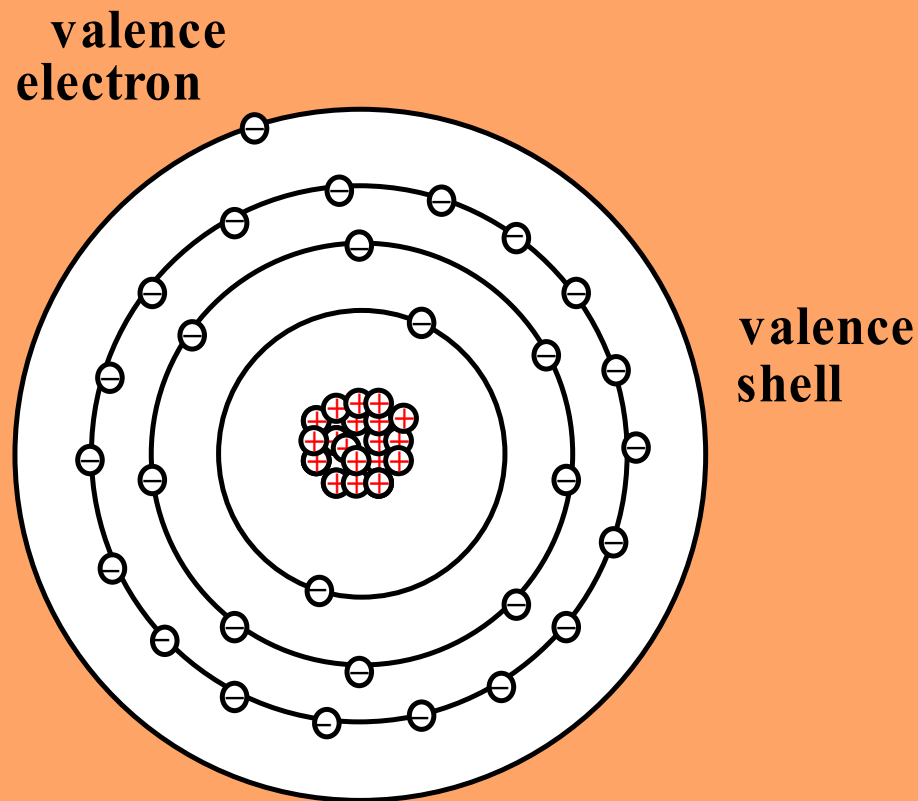
## Ohm's Law: Property of Resistance

Why are some materials better conductors than others? Consider copper.






# Basic Laws of Circuits
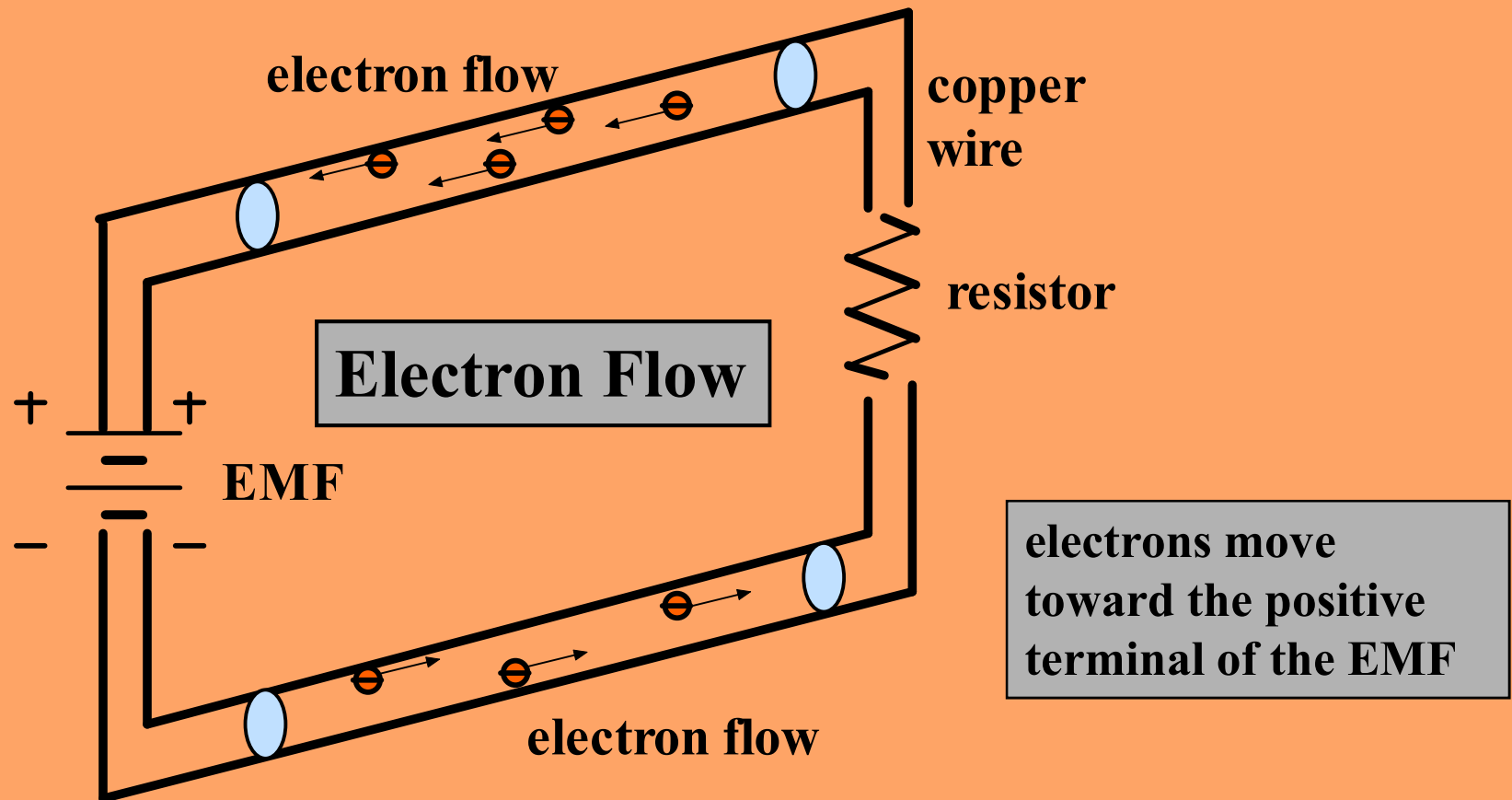
## Ohm's Law: Current


Under the influence of an electromotive force, the one valence electron of each copper atom is pulled from the outer orbit and moves through the copper space toward a positive potential.



# Basic Laws of Circuits
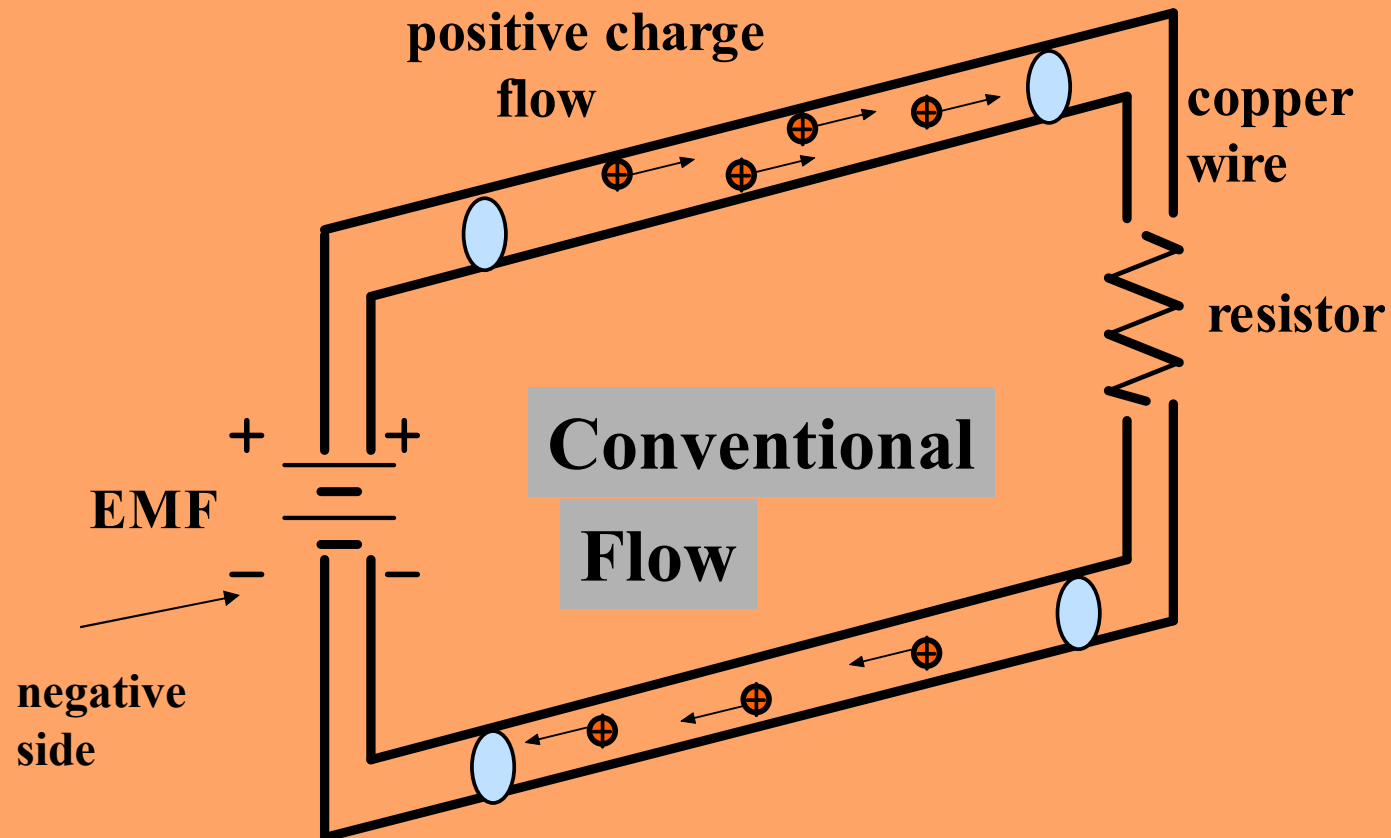
## Ohm's Law: Current

Conventional current flow assumes positive charges move toward the negative side of the circuit EMF.




# Basic Laws of Circuits
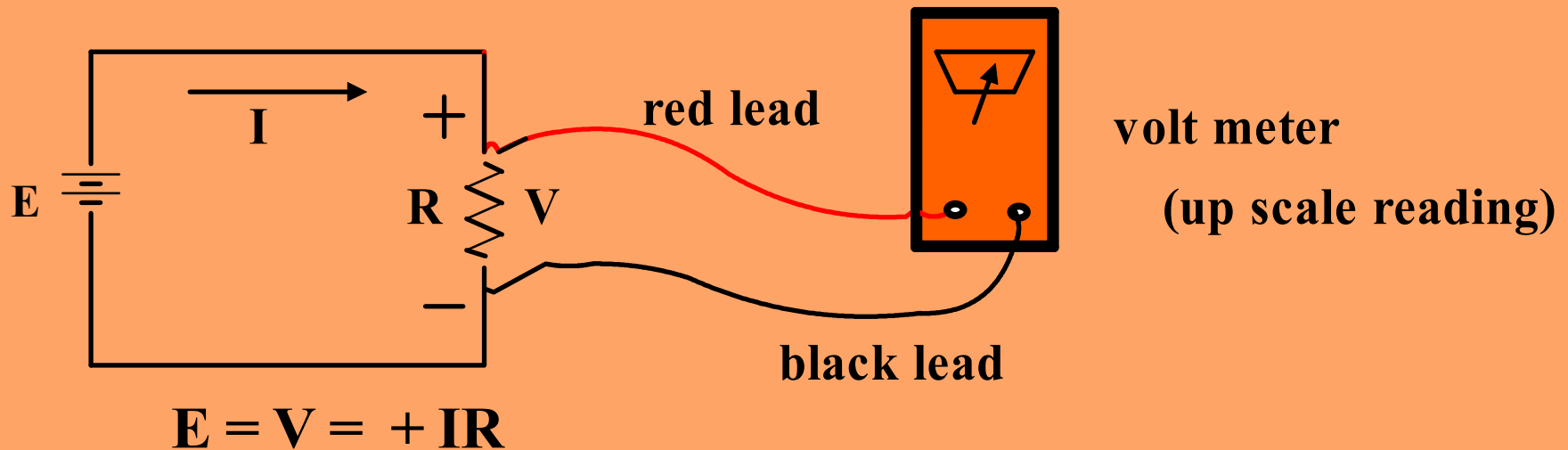
## Ohm's Law: Current

We assume conventional current flow (positive charge movement) although we know this is not the case.

Assuming conventional current flow does not change the answer(s) to an electric circuit solution.




# Basic Laws of Circuits
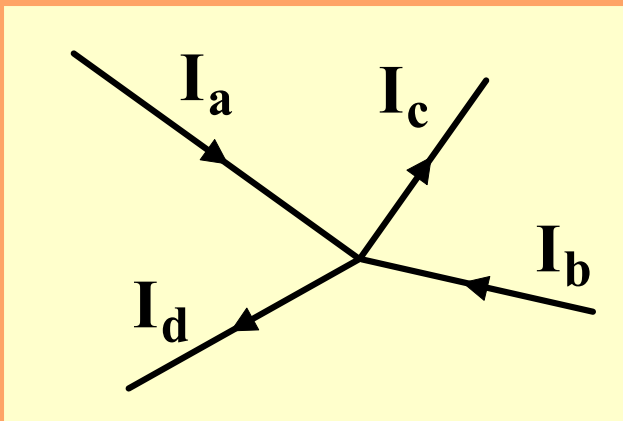
## Kirchhoff's Current Law

As a consequence of the Law of the conservation of charge, we have:

- The sum of the current entering a node (junction point) equal to the sum of the currents leaving.




$$I_a + I_b = I_c + I_d$$

$I_a$ ,  $I_b$ ,  $I_c$ , and  $I_d$  can each be either a positive or negative number.

# Basic Laws of Circuits
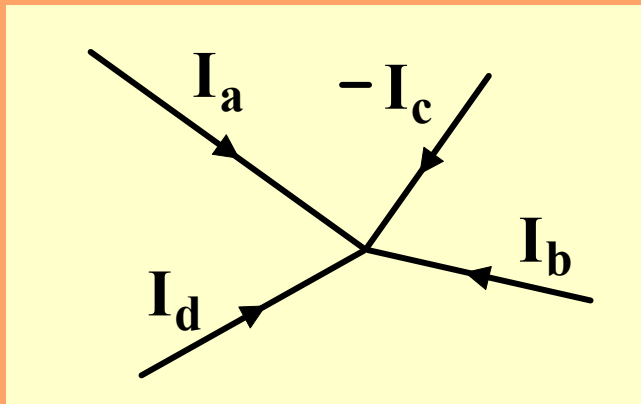
## Kirchhoff's Current Law

- The algebraic sum of the currents entering a node equal to zero.




$$I_a + I_b - I_c + I_d = 0$$

$I_a$ ,  $I_b$ ,  $I_c$ , and  $I_d$  can each be either a positive or negative number.

# Basic Laws of Circuits
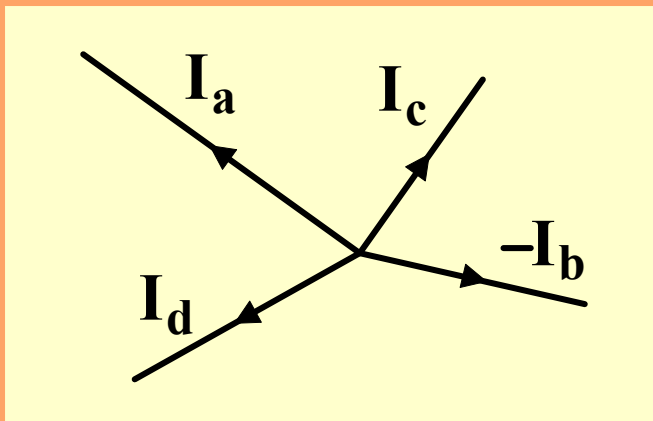
## Kirchhoff's Current Law

- The algebraic sum of the currents leaving a node equal to zero.




$$I_a - I_b + I_c + I_d = 0$$

$I_a$ ,  $I_b$ ,  $I_c$ , and  $I_d$  can each be either a positive or negative number.

# Basic Laws of Circuits

## Kirchhoff's Current Law: Example 2.2.

Find the current  $I_x$ .

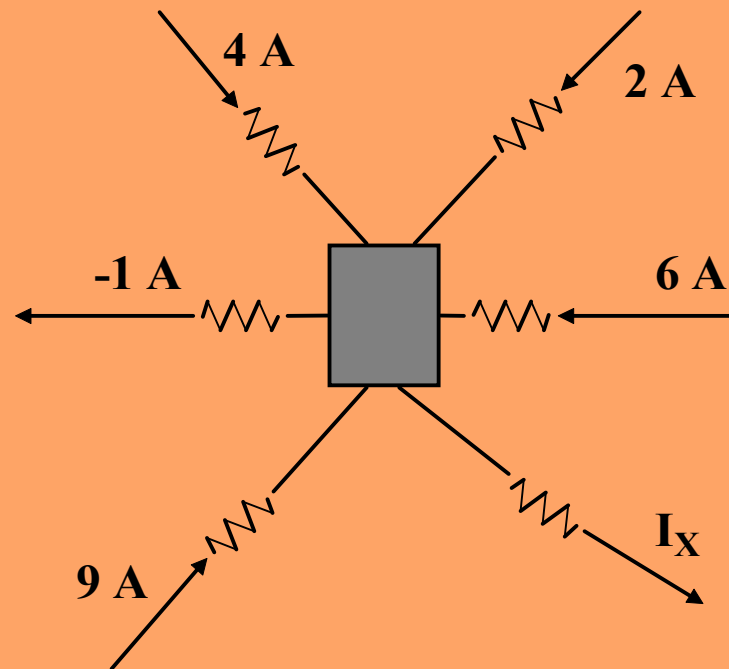


Ans:  $I_x =$

Highlight the box  
then use bring to  
front to see answer.

# Basic Laws of Circuits
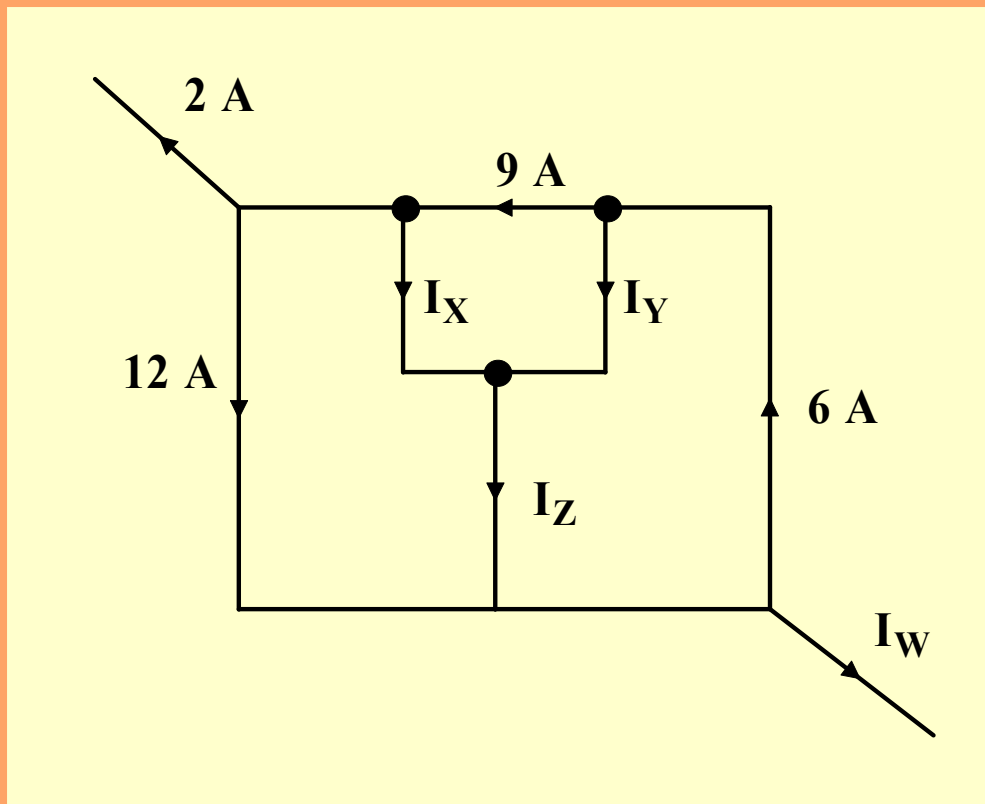
## Kirchhoff's Current Law: Example 2.3

Find the currents  $I_W$ ,  $I_X$ ,  $I_Y$ ,  $I_Z$ .



$$I_W = \boxed{\phantom{000}}$$

$$I_X = \boxed{\phantom{000}}$$

$$I_Y = \boxed{\phantom{000}}$$


$$I_Z = \boxed{\phantom{000}}$$



# Basic Laws of Circuits


## Kirchhoff's Current Law

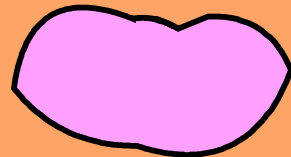**Kirchhoff's current law can be generalized to include a surface. We assume the elements within the surface are interconnected.**



**A closed 3D surface**

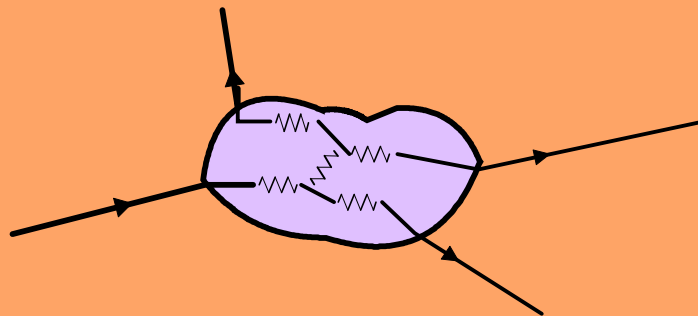**We can now apply Kirchhoff's current law in the 3 forms we discussed with a node. The appearance might be as follows:**




**Currents entering and leaving a closed surface that contains interconnected circuit elements**


# Basic Laws of Circuits
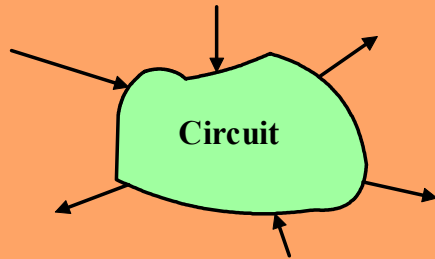
## Kirchhoff's Current Law


As a consequence of the Law of the conservation of charge, we have:


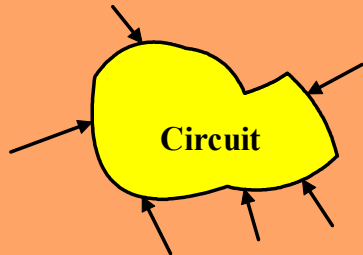
$$\sum_{j=1}^{j=N} i_j = \sum_{k=1}^{k=M} i_k$$



$$\sum_{r=1}^{r=Q} i_r = 0$$

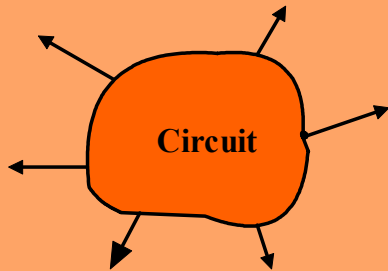


$$\sum_{m=1}^{m=Q} i_m = 0$$

# Basic Laws of Circuits
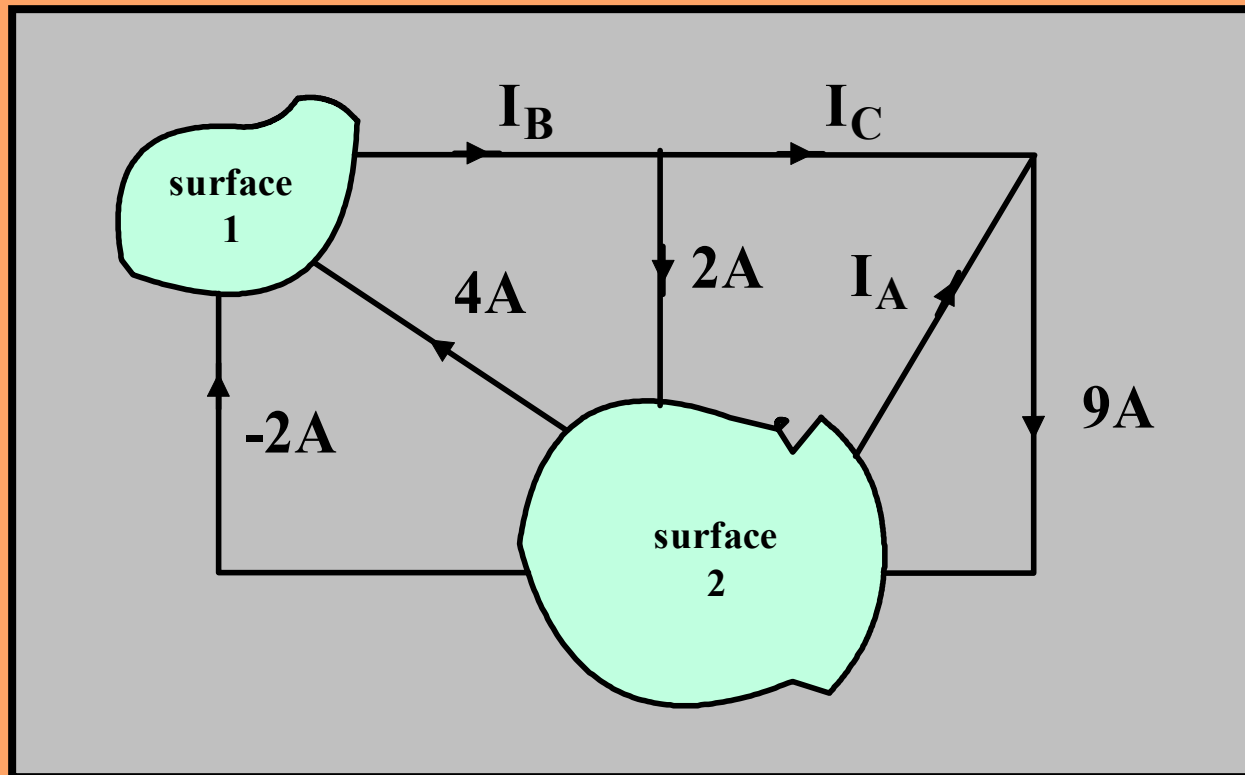
## Kirchhoff's Current Law: Example 2.4

Find the currents  $I_A$ ,  $I_B$ , and  $I_C$  in the circuit below.



# Basic Laws of Circuits

## Kirchhoff's Current Law: Solution for Example 2.4

At surface 1:  $I_B = 2A$ : At node 1,  $I_c = 0A$ : At node 2,  $I_A = 9A$

