


# Natural and Step Response of Series & Parallel RLC Circuits (Second-order Circuits)

## Objectives:


- ✓ Determine the response form of the circuit
- ✓ Natural response parallel RLC circuits
- ✓ Natural response series RLC circuits
- ✓ Step response of parallel and series RLC circuits
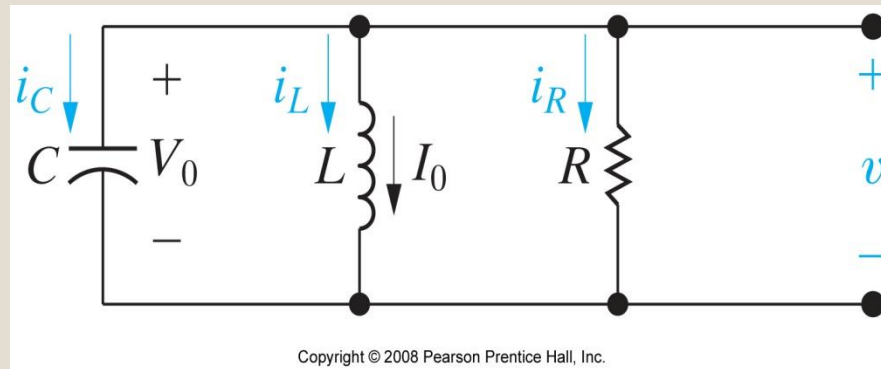
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .



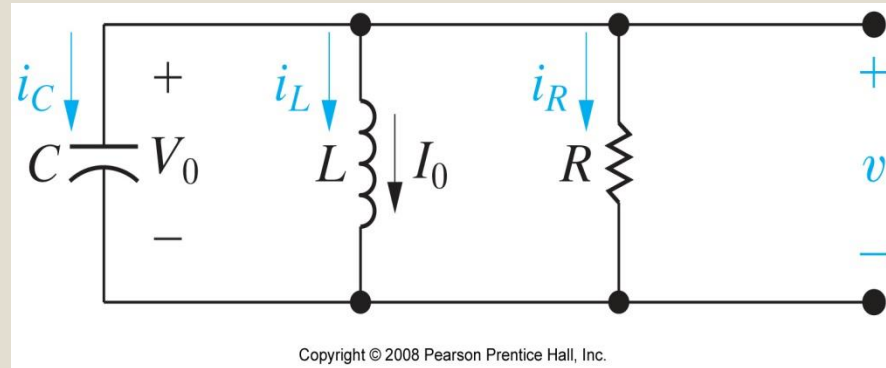
It is convenient to calculate  $v(t)$  for this circuit because



- X** A. The voltage must be continuous for all time
- X** B. The voltage is the same for all three components
- X** C. Once we have the voltage, it is pretty easy to calculate the branch current
- ✓** D. All of the above
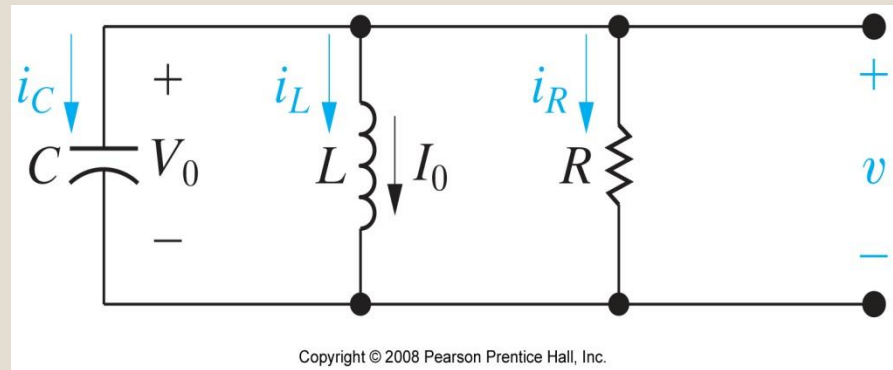
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .



$$\text{KCL: } C \frac{dv(t)}{dt} + \frac{1}{L} \int_0^t v(x) dx + I_0 + \frac{v(t)}{R} = 0$$

Differentiate both sides to remove the integral:


$$C \frac{d^2v(t)}{dt^2} + \frac{1}{L} v(t) + \frac{1}{R} \frac{dv(t)}{dt} = 0$$

Divide both sides by  $C$  to place in standard form:

$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC} v(t) + \frac{1}{RC} \frac{dv(t)}{dt} = 0$$
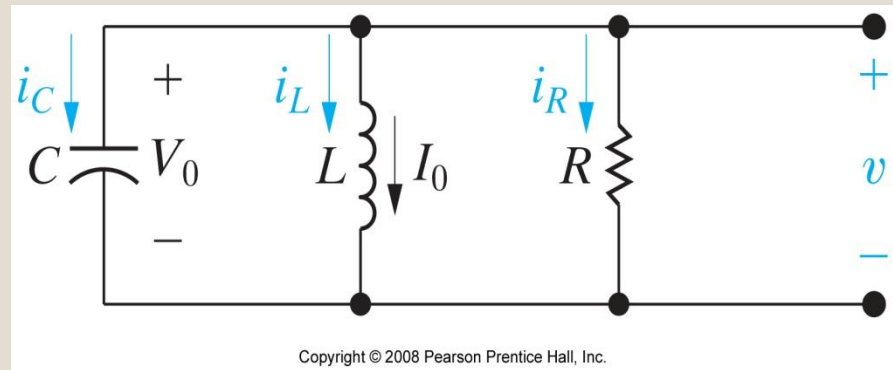
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .






Describing equation: 
$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC}v(t) + \frac{1}{RC}\frac{dv(t)}{dt} = 0$$

This equation is


- ✓ Second order
- ✓ Homogeneous
- ✓ Ordinary differential equation
- ✓ With constant coefficients

Once again we want to pick a possible solution to this differential equation. This must be a function whose first AND second derivatives have the same form as the original function, so a possible candidate is

-  A.  $K \sin \omega t$
-  B.  $Ke^{-at}$
-  C.  $Kt^2$
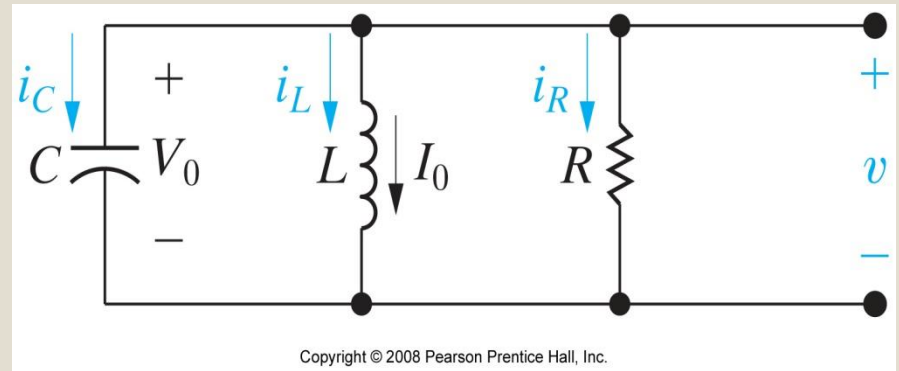
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .



Describing equation: 
$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC}v(t) + \frac{1}{RC}\frac{dv(t)}{dt} = 0$$

The circuit has two initial conditions that must be satisfied, so the solution for  $v(t)$  must have two constants. Use


$v(t) = A_1e^{s_1t} + A_2e^{s_2t}$  V;      Substitute:

$$(s_1^2 A_1 e^{s_1 t} + s_2^2 A_2 e^{s_2 t}) + \frac{1}{RC}(s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}) + \frac{1}{LC}(A_1 e^{s_1 t} + A_2 e^{s_2 t}) = 0$$

$$\Rightarrow [s_1^2 + (1/RC)s_1 + (1/LC)]A_1 e^{s_1 t} + [s_2^2 + (1/RC)s_2 + (1/LC)]A_2 e^{s_2 t} = 0$$
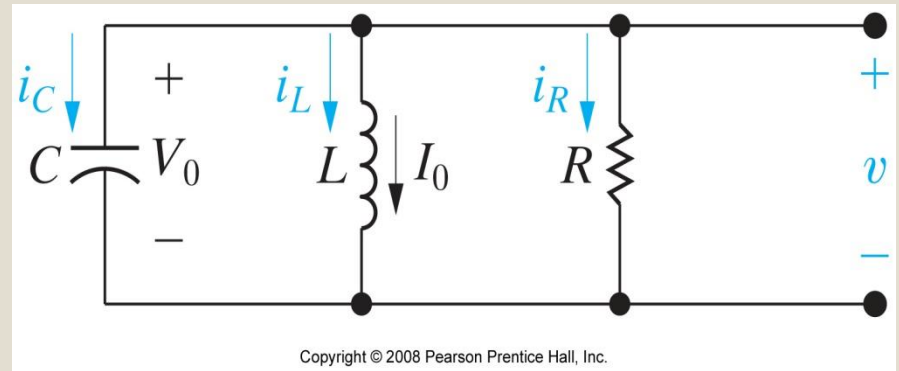
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .



Describing equation: 
$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC}v(t) + \frac{1}{RC}\frac{dv(t)}{dt} = 0$$

Solution: 
$$v(t) = A_1e^{s_1t} + A_2e^{s_2t}$$



Where  $s_1$  and  $s_2$  are solutions for the CHARACTERISTIC EQUATION:

$$s^2 + (1/RC)s + (1/LC) = 0$$




$$s^2 + (1/RC)s + (1/LC) = 0$$

is called the “characteristic equation” because it characterizes the circuit.

-  A. True
-  B. False
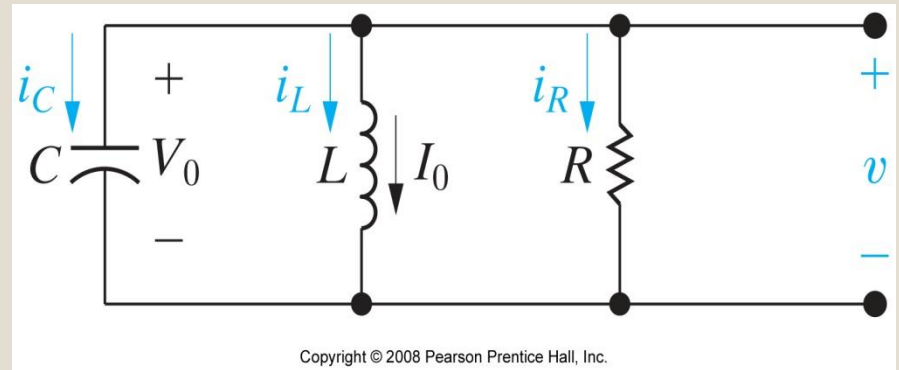
# Natural Response of Parallel RLC Circuits

The problem – given initial energy stored in the inductor and/or capacitor, find  $v(t)$  for  $t \geq 0$ .



The two solutions to the characteristic equation can be calculated using the quadratic formula:

$$s^2 + (1/RC)s + (1/LC) = 0; \quad s_{1,2} = \frac{-(1/RC) \pm \sqrt{(1/RC)^2 - 4(1/LC)}}{2}$$

$$s_{1,2} = -(1/2RC) \pm \sqrt{(1/2RC)^2 - (1/LC)} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where  $\alpha = \frac{1}{2RC}$  (the neper frequency in rad/s)




and  $\omega_0 = \sqrt{\frac{1}{LC}}$  (the resonant radian frequency in rad/s)

So far, we know that the parallel RLC natural response is given by

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \quad \text{where} \quad \alpha = \frac{1}{2RC} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

There are three different forms for  $s_1$  and  $s_2$ . For a parallel RLC circuit with specific values of R, L and C, the form for  $s_1$  and  $s_2$  depends on

-  A. The value of  $\alpha$
-  B. The value of  $\omega_0$
-  C. The value of  $(\alpha^2 - \omega_0^2)$
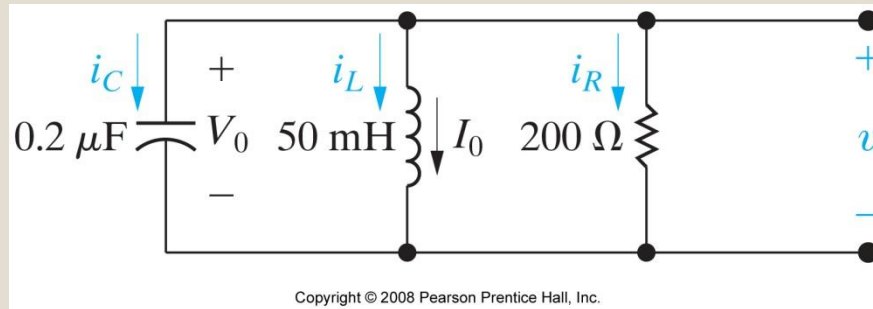
# Natural Response – Overdamped Example

Given  $V_0 = 12$  V and  $I_0 = 30$  mA, find  $v(t)$  for  $t \geq 0$ .



$$\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2\mu)} = 12,500 \text{ rad/s}$$


$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(0.05)(0.2\mu)}} = 10,000 \text{ rad/s}$$

$\alpha^2 > \omega_0^2$  so this is the overdamped case!

$$\begin{aligned} s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -12,500 \pm \sqrt{(12,500)^2 - (10,000)^2} \\ &= -12,000 \pm 7500 \quad \Rightarrow \quad s_1 = -5000 \text{ rad/s}, s_2 = -20,000 \text{ rad/s} \end{aligned}$$
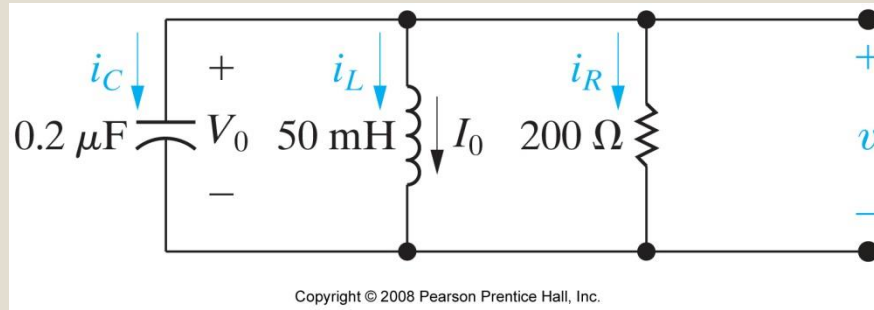
# Natural Response – Overdamped Example

Given  $V_0 = 12$  V and  $I_0 = 30$  mA, find  $v(t)$  for  $t \geq 0$ .



$$v(t) = A_1 e^{-5000t} + A_2 e^{-20,000t} \text{ V, for } t \geq 0$$


Now we must use the coefficients in the equation to satisfy the initial conditions in the circuit :

$$v(t) \Big|_{t=0} \text{ in the equation} = v(t) \Big|_{t=0} \text{ in the circuit}$$

$$\frac{dv(t)}{dt} \Big|_{t=0} \text{ in the equation} = \frac{dv(t)}{dt} \Big|_{t=0} \text{ in the circuit}$$
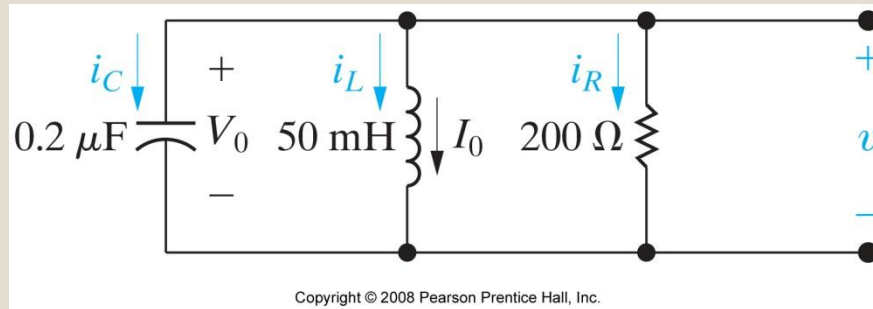
# Natural Response – Overdamped Example

Given  $V_0 = 12\text{ V}$  and  $I_0 = 30\text{ mA}$ , find  $v(t)$  for  $t \geq 0$ .






Equation: 
$$v(0) = A_1 e^{-5000(0)} + A_2 e^{-20,000(0)} = A_1 + A_2$$

Circuit: 
$$v(0) = V_0 = 12\text{ V}$$

$$\Rightarrow A_1 + A_2 = 12$$


Equation: 
$$\begin{aligned} \frac{dv(0)}{dt} &= (-5000)A_1 e^{-5000(0)} + (-20,000)A_2 e^{-20,000(0)} \\ &= -5000A_1 - 20,000A_2 \end{aligned}$$

Now we need the initial value of the first derivative of the voltage from the circuit. The describing equation of which circuit component involves  $dv(t)/dt$ ?

-  A. The resistor
-  B. The inductor
-  C. The capacitor
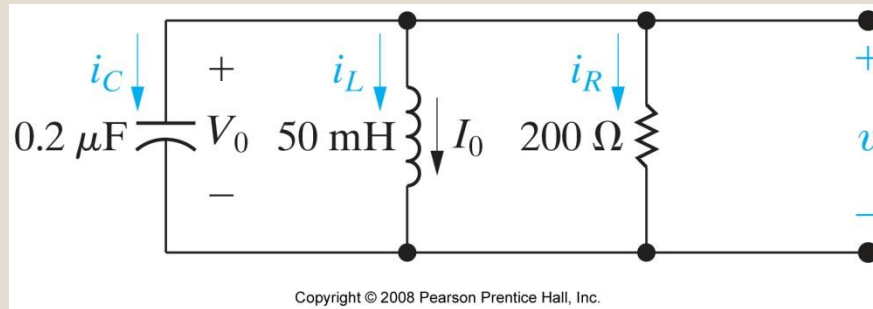
# Natural Response – Overdamped Example

Given  $V_0 = 12\text{ V}$  and  $I_0 = 30\text{ mA}$ , find  $v(t)$  for  $t \geq 0$ .



Equation: 
$$\frac{dv(0)}{dt} = (-5000)A_1 e^{-5000(0)} + (-20,000)A_2 e^{-20,000(0)}$$
$$= -5000A_1 - 20,000A_2$$


Circuit: 
$$i_C(t) = C \frac{dv(t)}{dt} \Rightarrow \frac{dv(0)}{dt} = \frac{1}{C} i_C(0) = \frac{1}{C} (-i_L(0) - i_R(0))$$

$$\frac{dv(0)}{dt} = \frac{1}{C} \left( -i_L(0) - \frac{v(0)}{R} \right) = \frac{1}{0.2\mu} \left( -0.03 - \frac{12}{200} \right) = -450,000\text{V/s}$$
$$\Rightarrow -5000A_1 - 20,000A_2 = -450,000$$


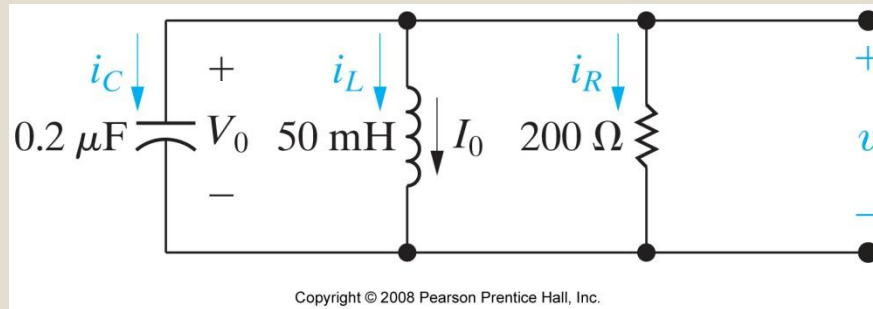
# Natural Response – Overdamped Example

Given  $V_0 = 12$  V and  $I_0 = 30$  mA, find  $v(t)$  for  $t \geq 0$ .



$$v(t) = A_1 e^{-5000t} + A_2 e^{-20,000t} \text{ V, for } t \geq 0$$

$$A_1 + A_2 = 12; \quad -5000A_1 - 20,000A_2 = -450,000$$

$$\text{Solving simultaneously, } A_1 = -14, \quad A_2 = 26$$

Thus,


$$v(t) = -14e^{-5000t} + 26e^{-20,000t} \text{ V, for } t \geq 0$$

$$\text{Checks: } v(0) = -14 + 26 = 12 \text{ V (OK)}$$

$$v(\infty) = 0 \text{ (OK)}$$
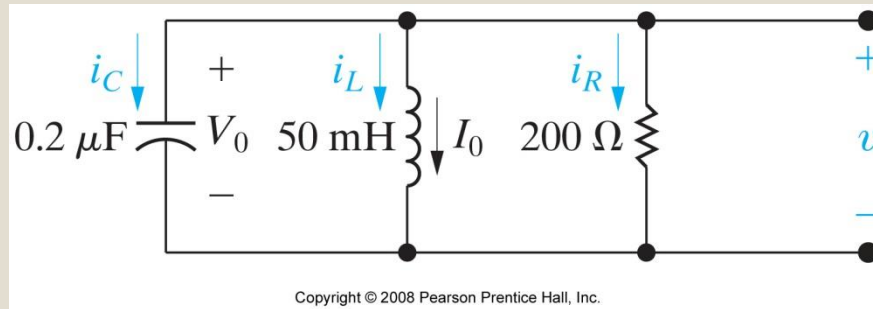
# Natural Response – Overdamped Example

Given  $V_0 = 12\text{ V}$  and  $I_0 = 30\text{ mA}$ , find  $v(t)$  for  $t \geq 0$ .



You can solve this problem using the Second-Order Circuits table:

1. Make sure you are on the Natural Response side.
2. Find the parallel RLC column.
3. Use the equations in Row 4 to calculate  $\alpha$  and  $\omega_0$ .
4. Compare the values of  $\alpha$  and  $\omega_0$  to determine the response form (given in one of the last 3 rows).
5. Use the equations to solve for the unknown coefficients.
6. Write the equation for  $v(t)$ ,  $t \geq 0$ .
7. Solve for any other quantities requested in the problem.