

# CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

## Condition for maximum power transfer

Suppose we can vary the load resistance. For what value of load resistance will maximum power be absorbed by the load?

$$p_L = i^2 R_L; \quad i = \frac{V_{Th}}{R_{Th} + R_L}$$


$$\therefore p_L = \frac{R_L V_{Th}^2}{(R_{Th} + R_L)^2}$$

$$\text{For max. power, } \frac{dp_L}{dR_L} = 0$$

$$\begin{aligned} \frac{dp_L}{dR_L} &= \frac{V_{Th}^2}{(R_{Th} + R_L)^2} - \frac{2R_L V_{Th}^2}{(R_{Th} + R_L)^3} \\ &= \frac{V_{Th}^2 (R_{Th} + R_L) - 2R_L V_{Th}^2}{(R_{Th} + R_L)^3} = 0 \end{aligned}$$

$$\Rightarrow V_{Th}^2 (R_{Th} + R_L) - 2R_L V_{Th}^2 = 0$$
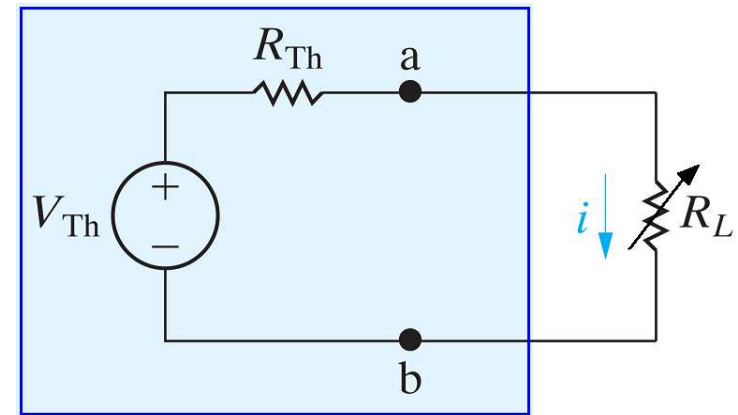
$$\Rightarrow (R_{Th} + R_L) = 2R_L \quad \therefore R_L = R_{Th}$$




Represents the  
Thevenin equivalent  
of an arbitrary  
subcircuit that will  
not change

Represents  
a variable  
load



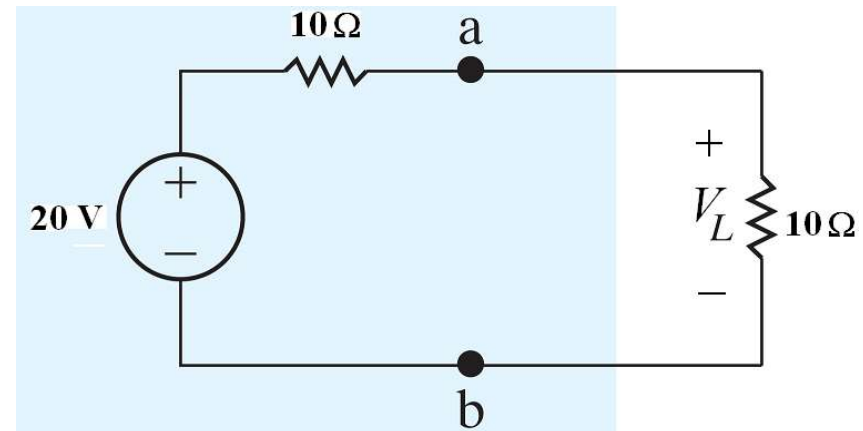
IN THE CIRCUIT BELOW, THE LOAD RESISTOR IS MATCHED TO THE THEVENIN RESISTANCE – HOW MUCH VOLTAGE DROPS ACROSS THE LOAD RESISTOR?



- X** A. 20 V
- ✓** B. 10 V
- X** C. 5 V
- X** D. 40 V



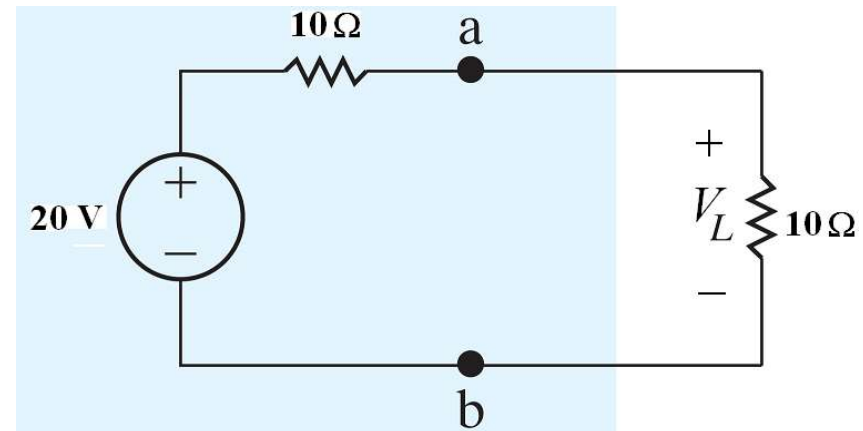
IN THE CIRCUIT BELOW, THE LOAD RESISTOR IS MATCHED TO THE THEVENIN RESISTANCE – HOW MUCH POWER IS ABSORBED BY THE LOAD RESISTOR?



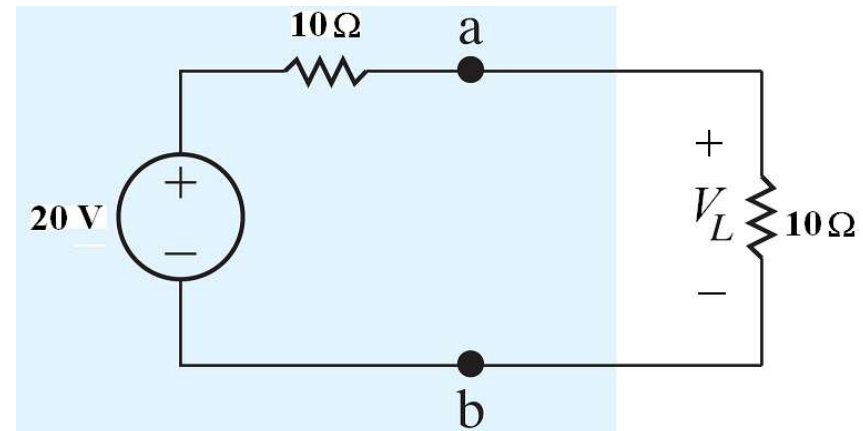- A. 100 W
- B. 50 W
- C. 20 W
- D. 10 W




IN THE CIRCUIT BELOW, THE LOAD RESISTOR IS MATCHED TO THE THEVENIN RESISTANCE – HOW MUCH POWER IS DELIVERED BY THE VOLTAGE SOURCE?



- X** A. 100 W
- X** B. 50 W
- ✓** C. 20 W
- X** D. 10 W



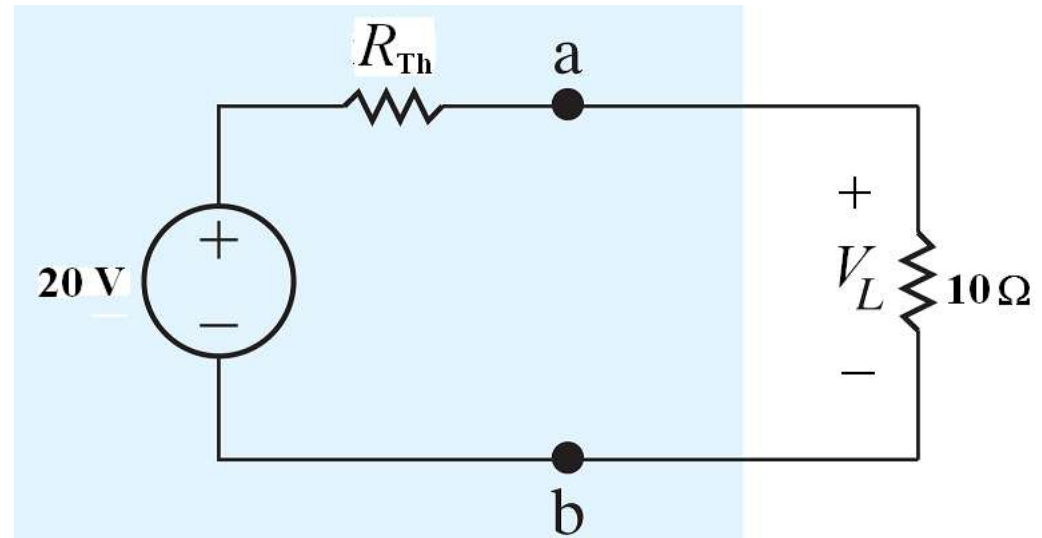SUPPOSE THAT WE VARY THE THEVENIN RESISTOR INSTEAD OF THE LOAD RESISTOR. FOR WHAT VALUE OF THEVENIN RESISTANCE IS MAXIMUM POWER DELIVERED TO THE LOAD RESISTANCE?




- A.  $20\ \Omega$
- B.  $10\ \Omega$
- C.  $0\ \Omega$
- D. None of the above



## CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS
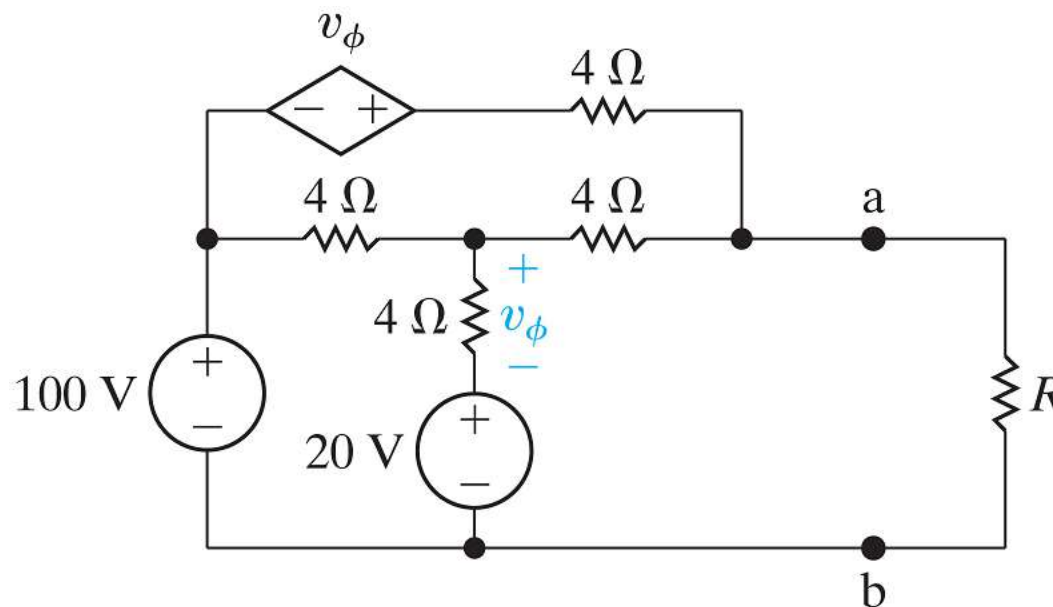
### Example of maximum power transfer

Find the value of  $R$  such that maximum power is transferred to  $R$ , and find that maximum power.




Approach – find the open circuit and the short circuit current by analyzing two circuits – see the next slides.



## CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Find the value of R such that maximum power is transferred to R, and find that maximum power.

Find the open circuit voltage:

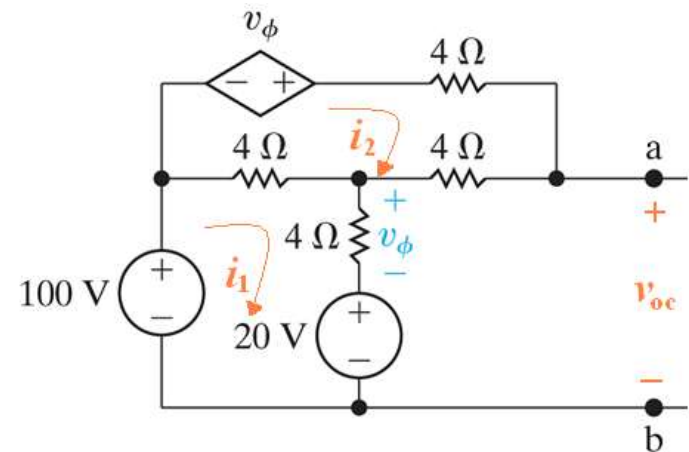

$$i_1 \text{ mesh : } -100 + 4(i_1 - i_2) + 4i_1 + 20 = 0$$

$$i_2 \text{ mesh : } -v_\phi + 4i_2 + 4(i_2 - i_1) = 0$$

$$\text{constraint : } v_\phi = 4i_1$$

$$\text{Solving : } i_1 = 15 \text{ A; } \quad i_2 = 10 \text{ A; } \quad v_\phi = 60 \text{ V}$$


$$\therefore v_{oc} = 4i_2 + 4i_1 + 20 = 120 \text{ V}$$



## CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Find the value of  $R$  such that maximum power is transferred to  $R$ , and find that maximum power.

Find the short circuit current:

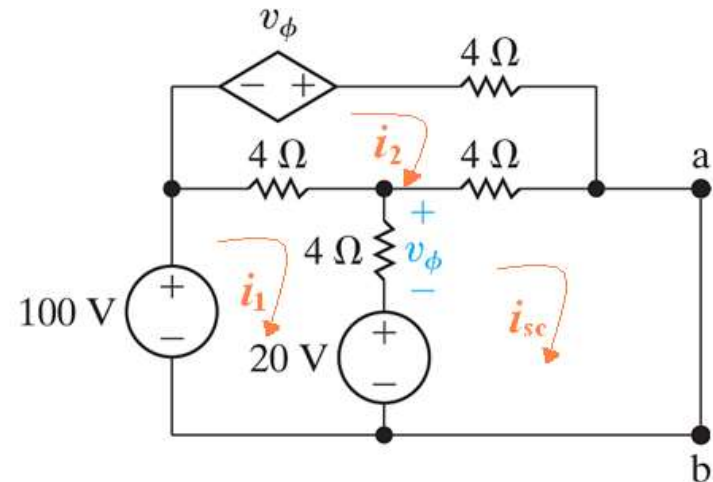

$$i_1 \text{ mesh : } -100 + 4(i_1 - i_2) + 4(i_1 - i_{sc}) + 20 = 0$$

$$i_2 \text{ mesh : } -v_\phi + 4i_2 + 4(i_2 - i_{sc}) + 4(i_2 - i_1) = 0$$

$$i_{sc} \text{ mesh : } -20 + 4(i_{sc} + i_1) + 4(i_{sc} - i_2) = 0$$

$$\text{constraint : } v_\phi = 4(i_1 - i_{sc})$$

$$\text{Solving : } i_1 = 45 \text{ A; } \quad i_2 = 30 \text{ A; } \quad i_{sc} = 40 \text{ A; } \quad v_\phi = 20 \text{ V}$$

$$\therefore R_{Th} = \frac{v_{oc}}{i_{sc}} = \frac{120}{40} = 3\Omega$$






## CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Find the value of R such that maximum power is transferred to R, and find that maximum power.

The Thevenin equivalent:

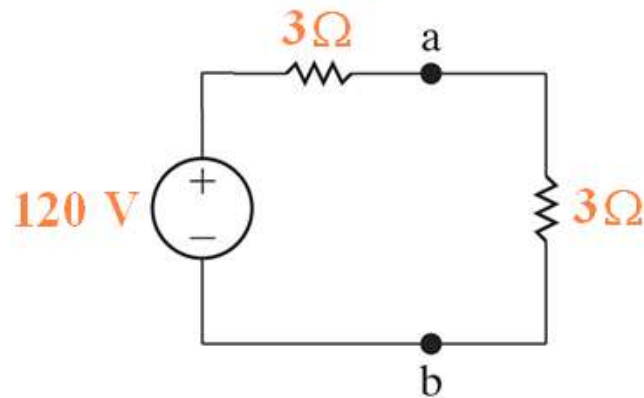

$$p_L = \frac{60^2}{3} = 1200 \text{ W}$$



# CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Summary of circuit analysis techniques:

- Ohm's Law
- KVL and KCL
- Combining resistors in series and parallel
- Voltage division and current division
- Node voltage method
- Mesh current method
- Source transformation
- Thevenin and Norton equivalents

