

CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Objectives:

- Know how to use the node voltage method to solve a circuit
- Know how to use the mesh current method to solve a circuit
- Be able to choose the appropriate circuit analysis method to use for a particular circuit
- Know how to use source transformation to simplify a circuit
- Be able to calculate the Thevenin and Norton equivalents for a circuit
- Understand and be able to use the condition for maximum power transfer to a load



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS


Terminology:

- Node – a point where two or more circuit elements are joined
- Essential node – a point where three or more circuit elements are joined
- Loop – a path whose ending node is the same as its starting node, and does not contain any intermediate nodes more than once
- Mesh – a loop that does not contain any other loops




CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

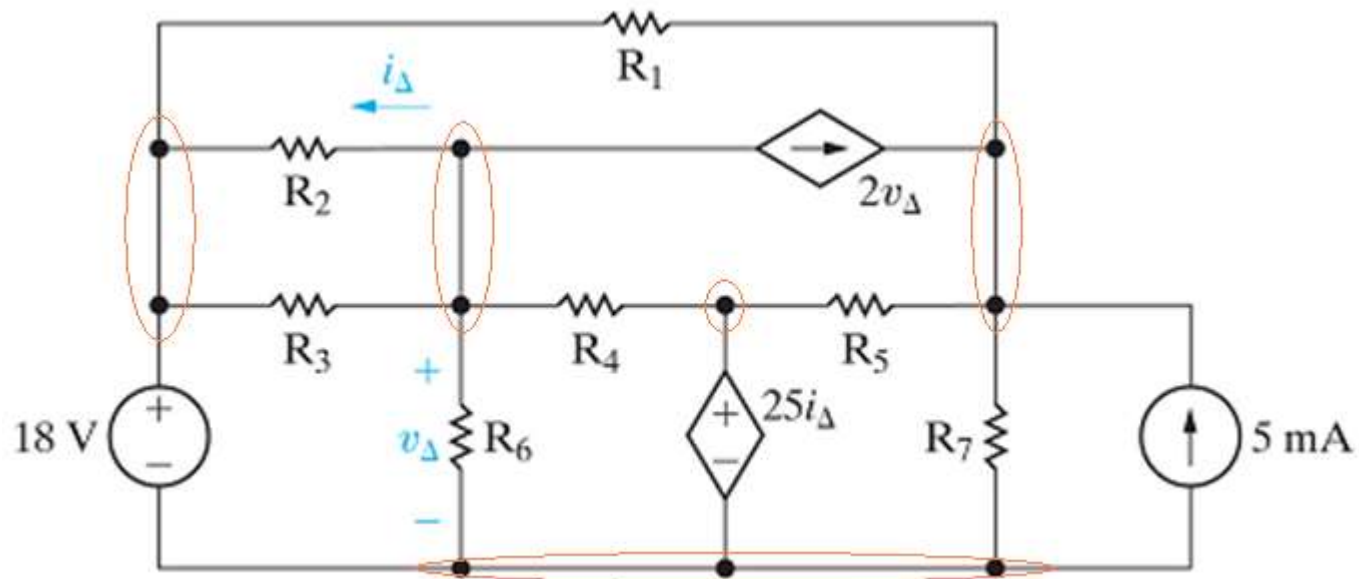Identify all of the nodes in this circuit.



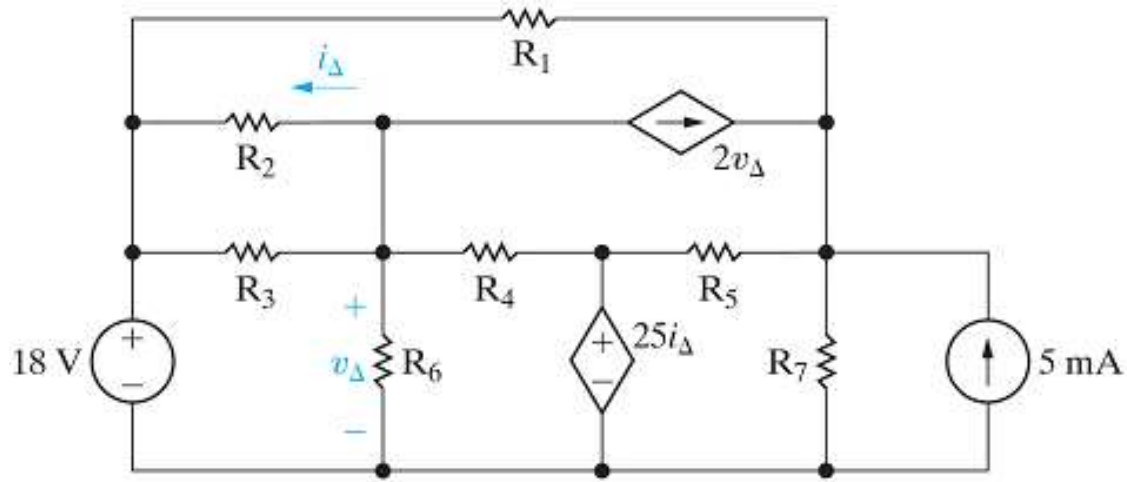HOW MANY ESSENTIAL NODES DOES THIS CIRCUIT HAVE?




- X** A. 4
- ✓** B. 5
- X** C. 7
- X** D. 10



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

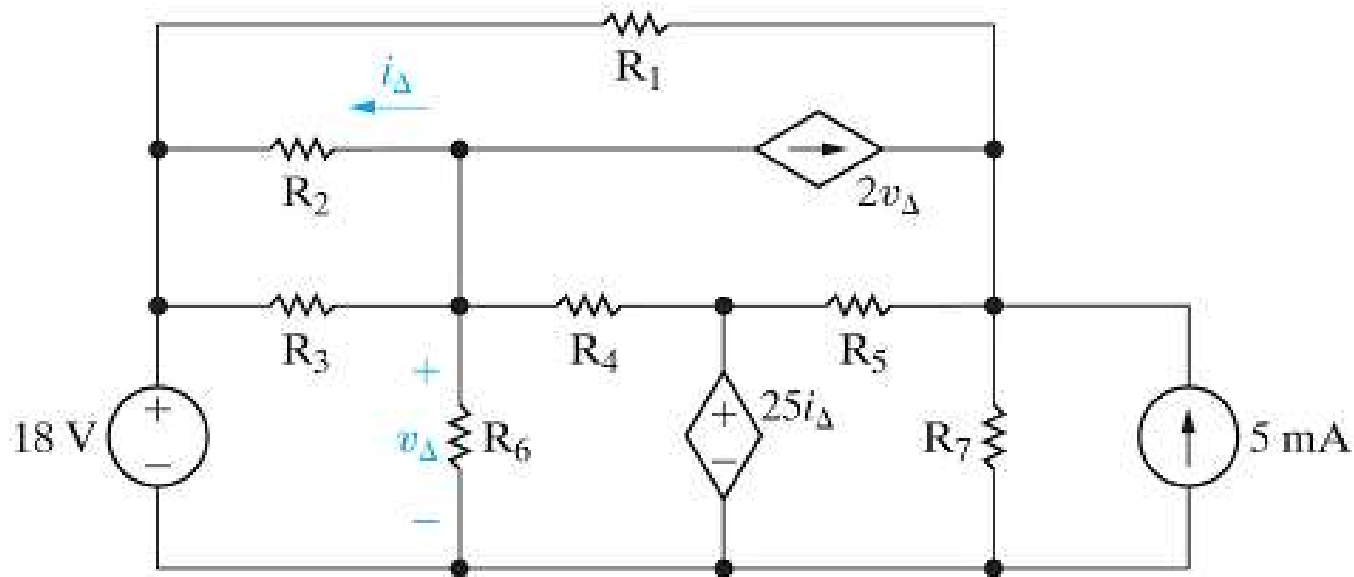
Identify all of the loops in this circuit.



R_1 , dep. source, R_2
 R_1 , R_5 , R_4 , R_2
Dep. Source, R_4 , R_5
 R_2 , dep. source, R_5 , R_4 , R_3
Etc . . .



HOW MANY MESHES DOES THIS CIRCUIT HAVE?

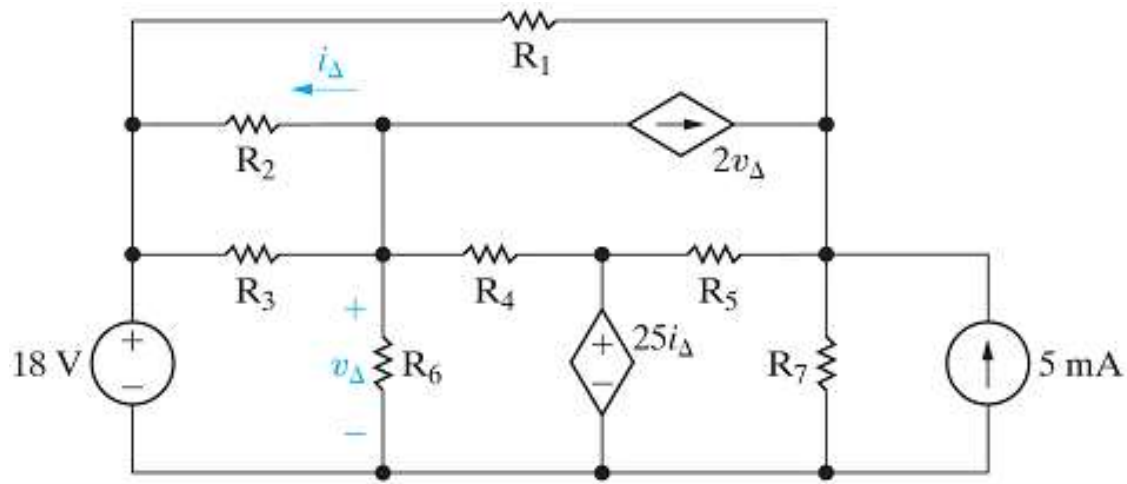

- X** A. 4
- X** B. 5
- ✓** C. 7
- X** D. 10



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:


- Based on writing KCL equations at essential nodes
- Solves for node voltages
- The “recipe”:
 1. Identify the essential nodes
 2. Pick a reference node
 3. Label remaining essential nodes with voltage values
 4. Write a KCL equation at each non-reference essential node
 5. Put equations in standard form and solve
 6. Check your solutions by balancing power
 7. Calculate quantities of interest



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:


Step 1 – identify the essential nodes

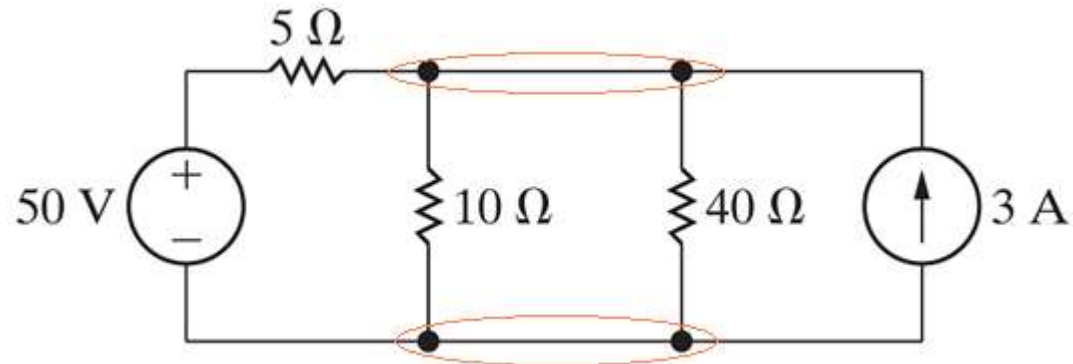

CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:


Step 2 – pick a reference node

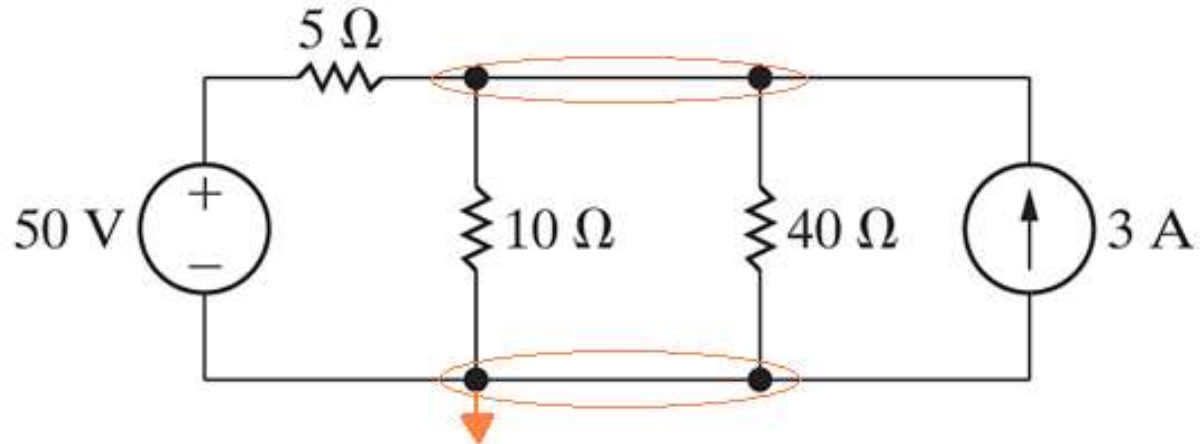

CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:


Step 3 – label the remaining essential nodes with voltage values

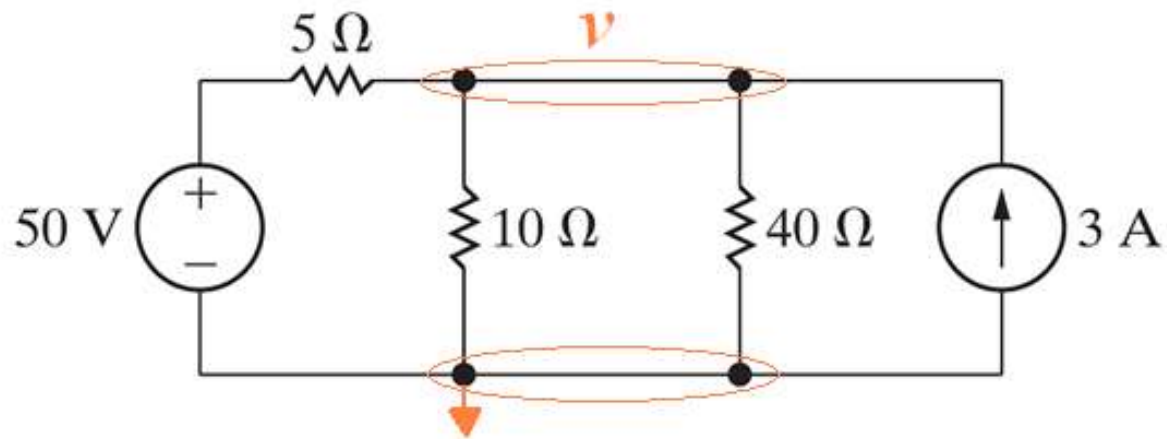

CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:

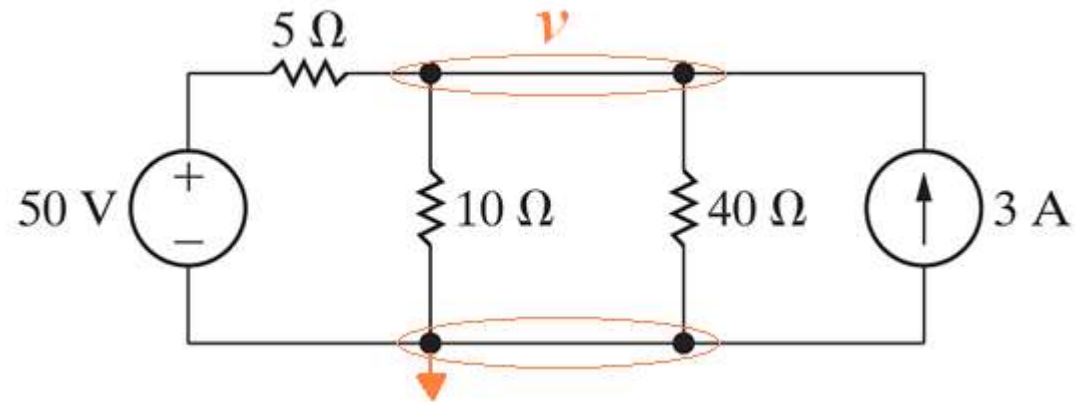Step 4 – write a KCL equation at each non-reference essential node




$$\text{At } v: \frac{v - 50}{5} + \frac{v - 0}{10} + \frac{v - 0}{40} - 3 = 0$$



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:

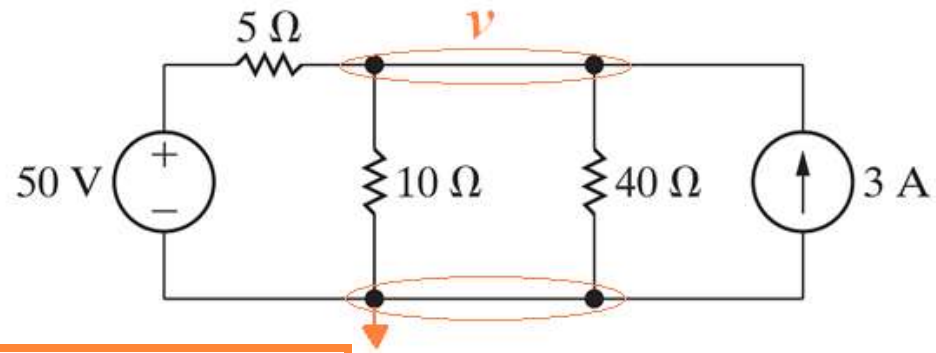Step 5 – put the equations in standard form and solve



$$\frac{v-50}{5} + \frac{v-0}{10} + \frac{v-0}{40} - 3 = 0$$

$$\Rightarrow v \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{40} \right) = 3 + \frac{50}{5}$$

$$\Rightarrow (40) \left[v \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{40} \right) \right] = (40) \left[3 + \frac{50}{5} \right]$$

$$\Rightarrow v(8 + 4 + 1) = 120 + 400$$


$$\Rightarrow v = 520/13 = 40 \text{ V}$$



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:

Step 6 – check your solutions

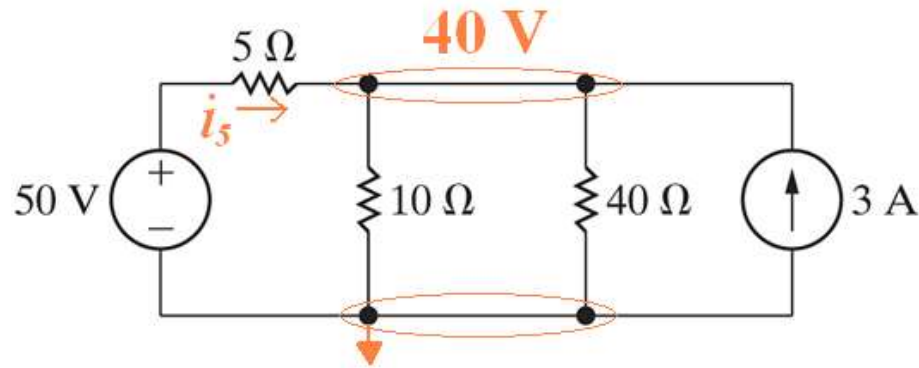

$$i_5 = \frac{50 - 40}{5} = 2 \text{ A} \quad p_{50} = -(50)(2) = -100 \text{ W}$$

$$p_5 = 5(2)^2 = 20 \text{ W} \quad p_{10} = (40)^2 / 10 = 160 \text{ W}$$

$$p_{40} = (40)^2 / 40 = 40 \text{ W} \quad p_3 = -(40)(3) = -120 \text{ W}$$


$$\sum p = -100 + 20 + 160 + 40 - 120 = 0$$



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:

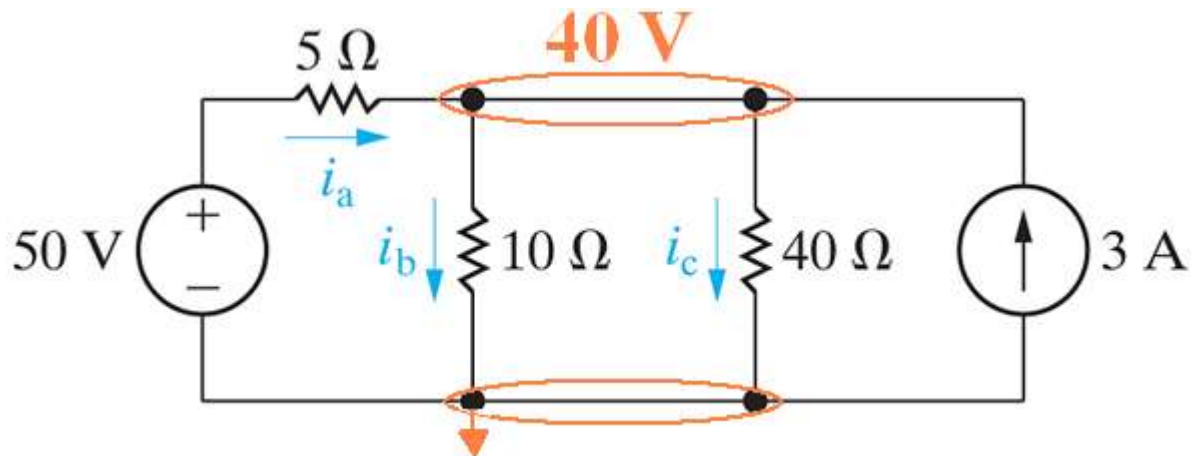Step 7 – calculate any other quantities of interest




$$i_a = \frac{50 - 40}{5} = 2 \text{ A}$$

$$i_b = \frac{40 - 0}{10} = 4 \text{ A}$$

$$i_c = \frac{40 - 0}{40} = 1 \text{ A}$$

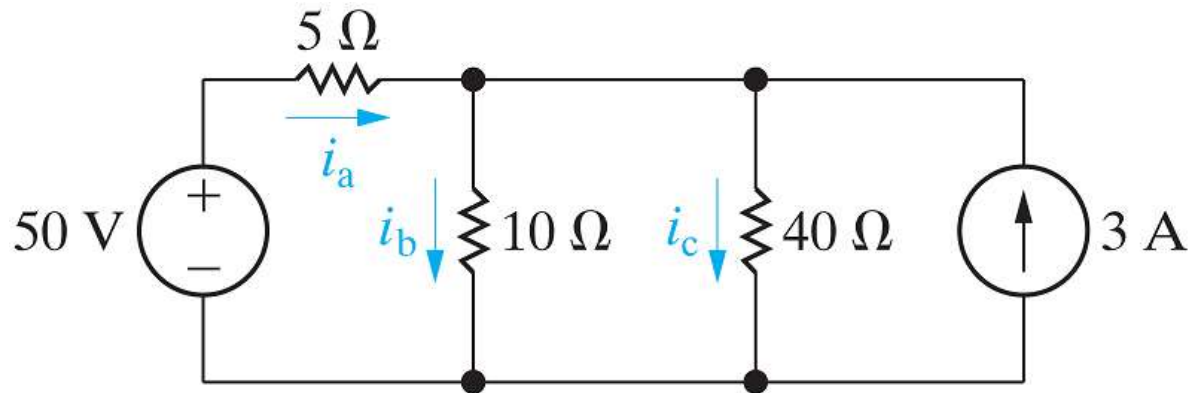WE JUST SHOWED THAT THE VOLTAGE DROP BETWEEN THE TOP NODE AND THE REFERENCE NODE IN THIS CIRCUIT IS 40 V. FIND i_C




- X** A. 2 A
- X** B. 4 A
- ✓** C. 1 A
- X** D. -1 A



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method:

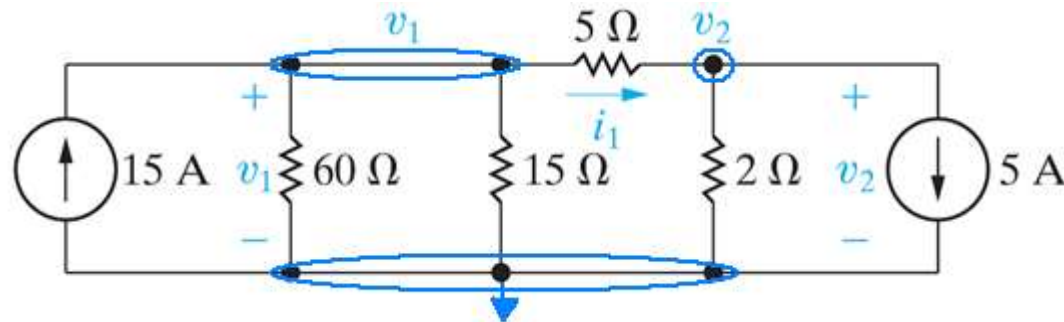Find the two voltages and the current indicated.



$$\text{At } v_1 : -15 + \frac{v_1}{60} + \frac{v_1}{15} + \frac{v_1 - v_2}{5} = 0$$

$$\text{At } v_2 : \frac{v_2 - v_1}{5} + \frac{v_2}{2} + 5 = 0$$

$$\text{Standard form : } v_1 \left(\frac{1}{60} + \frac{1}{15} + \frac{1}{5} \right) + v_2 \left(-\frac{1}{5} \right) = 15$$

$$v_1 \left(-\frac{1}{5} \right) + v_2 \left(\frac{1}{5} + \frac{1}{2} \right) = -5$$


$$\text{Calculator solution : } v_1 = 60 \text{ V; } v_2 = 10 \text{ V}$$



CHAPTER 4 – TECHNIQUES OF CIRCUIT ANALYSIS

Node voltage method (continued):

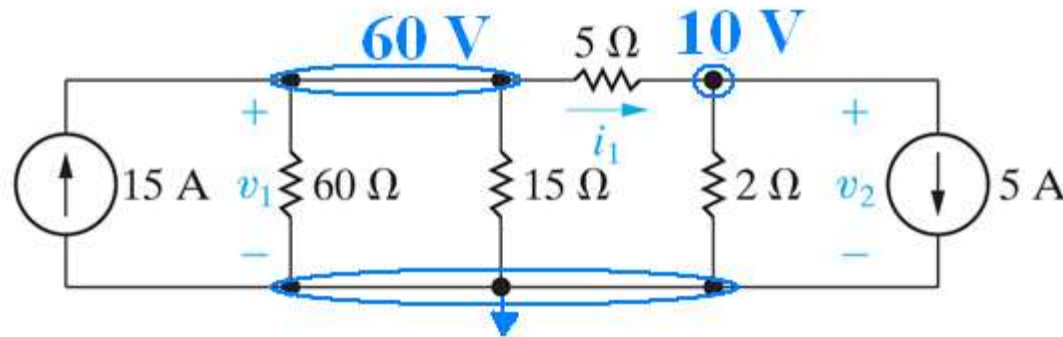Find the two voltages and the current indicated.



Power check :

$$p_{15A} = -(15)(60) = -900 \text{ W}; \quad p_{60} = \frac{60^2}{60} = 60 \text{ W};$$

$$p_{15\Omega} = \frac{60^2}{15} = 240 \text{ W}; \quad p_5 = \frac{(60-10)^2}{5} = 500 \text{ W};$$


$$p_2 = \frac{10^2}{2} = 50 \text{ W}; \quad p_{5A} = (5)(10) = 50 \text{ W}$$

$$\sum p = -900 + 60 + 240 + 500 + 50 + 50 = 0$$

$$\text{Calculate } i_1 : \quad i_1 = \frac{(60-10)}{5} = 10 \text{ A}$$



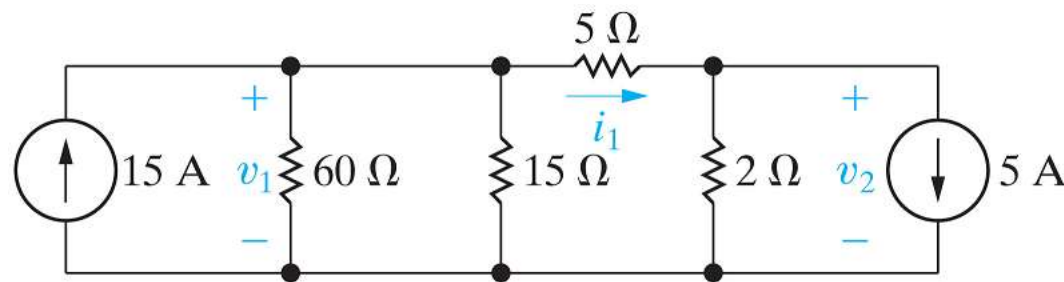
IF v_1 IS 60 V AND v_2 IS 10 V, WHAT IS THE POWER ASSOCIATED WITH THE 60 Ω RESISTOR?



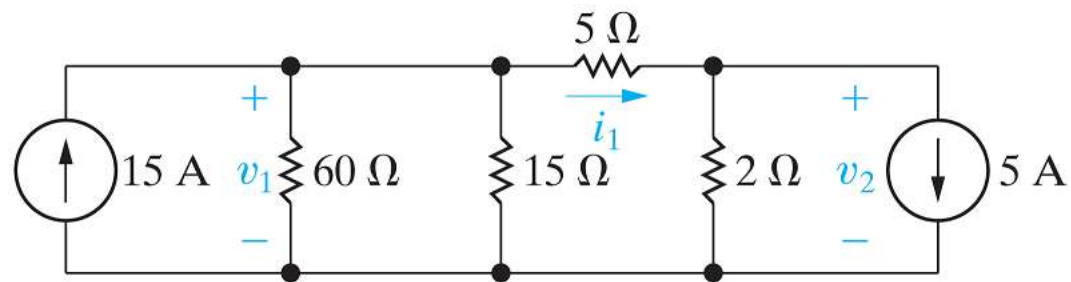- A. 60 W
- B. 240 W
- C. 3600 W
- D. None of the above



IF v_1 IS 60 V AND v_2 IS 10 V, WHAT IS THE POWER ASSOCIATED WITH THE 5 A SOURCE?



- X** A. 900 W
- X** B. -900 W
- X** C. -50 W
- ✓** D. 50 W

